

Chapter 2

Understanding Electrical Drawings

PART 5 Manual and Magnetic Motor Starters

© 2010, The McGraw-Hill Companies, Inc.

MANUAL MOTOR STARTER

© 2010, The McGraw-Hill Companies, Inc.

Manual motor starters are a very basic way to supply power to a motor. A manual control circuit is a circuit that requires the operator to control the motor directly at the location of the starter.



© 2010, The McGraw-Hill Companies, Inc.




Manual starters are operated by the manual start/stop mechanism located on the front of the starter enclosure. The start/stop mechanism moves all three contacts at once to close (start) or open (stop) the circuit to the motor.

Manual three-phase starters are used in low horsepower applications such as drill presses and table saws where remote push button control is not required.




© 2010, The McGraw-Hill Companies, Inc.

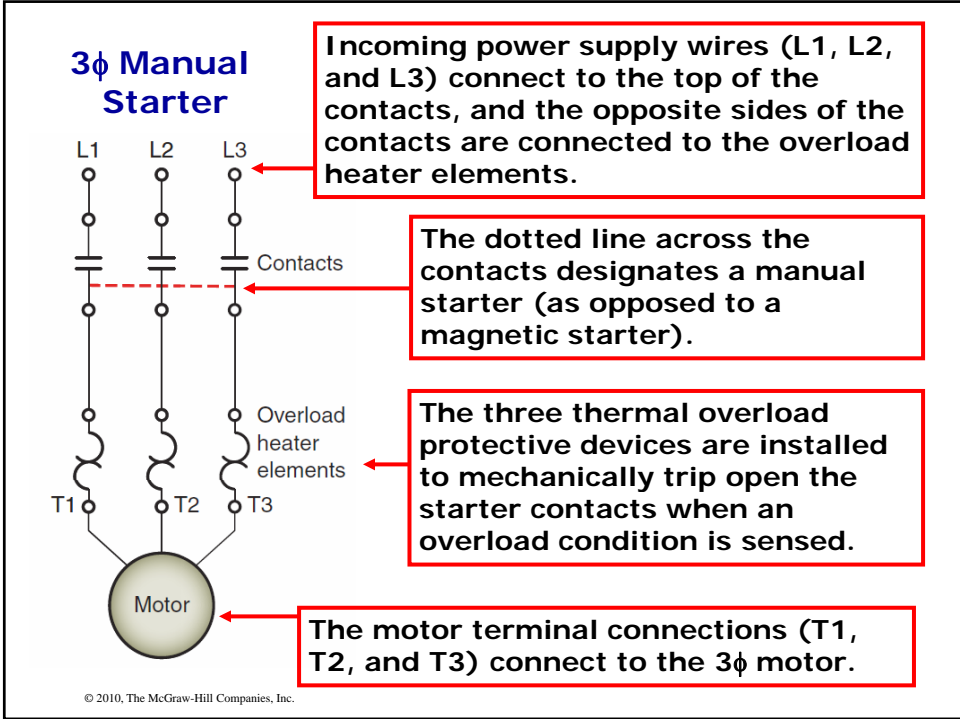

MAGNETIC MOTOR STARTER



© 2010, The McGraw-Hill Companies, Inc.

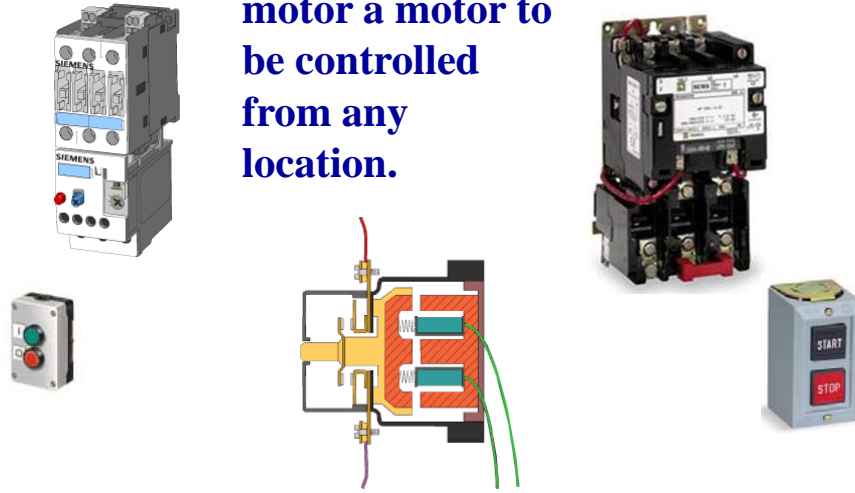Magnetic motor starters allow a motor a motor to be controlled from any location.




© 2010, The McGraw-Hill Companies, Inc.

3 ϕ Across-The-Line Magnetic Starter

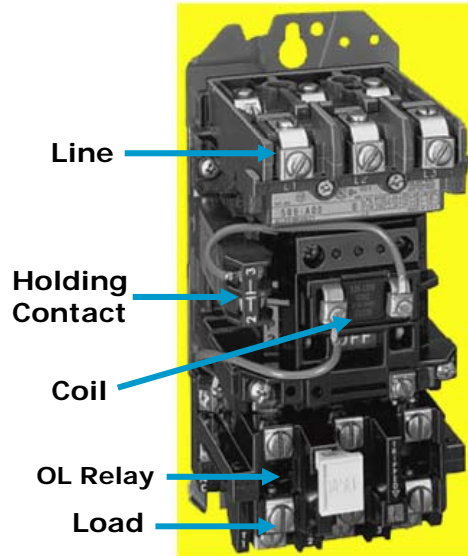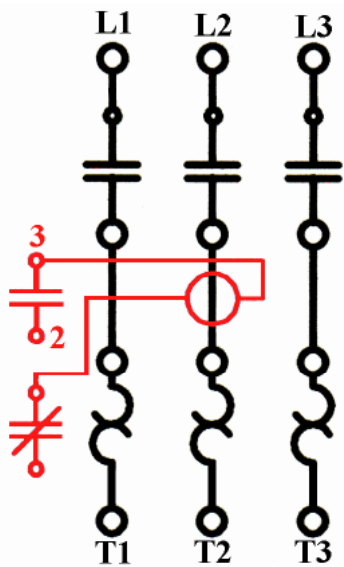

© 2010, The McGraw-Hill Companies, Inc.

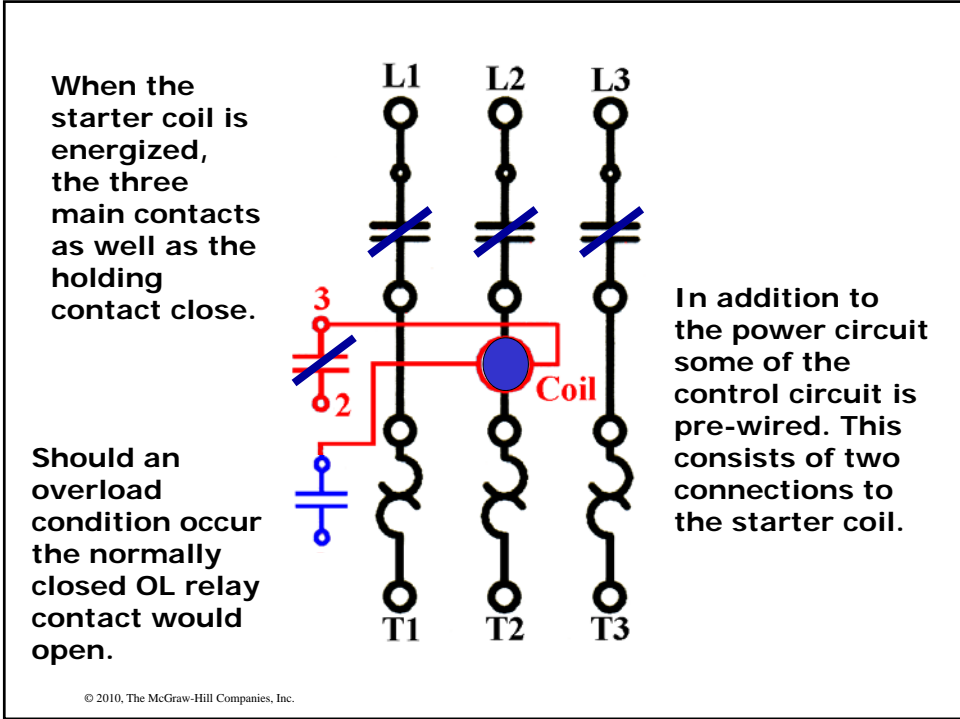


TWO-WIRE CONTROL CIRCUIT


© 2010, The McGraw-Hill Companies, Inc.

Magnetic motor control circuits are divided into two basic types: the two-wire control circuit, and the three-wire control circuit

Two-wire control

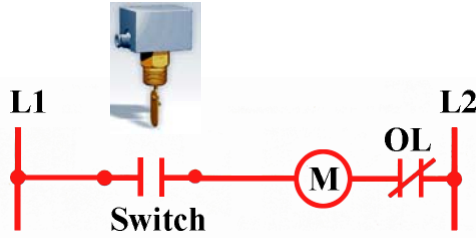

Three-wire control

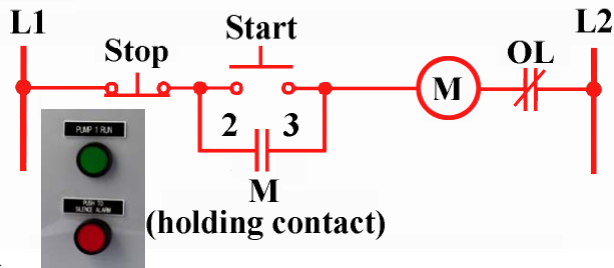


© 2010, The McGraw-Hill Companies, Inc.

Two-Wire Control Circuit




Remote pressure control switch

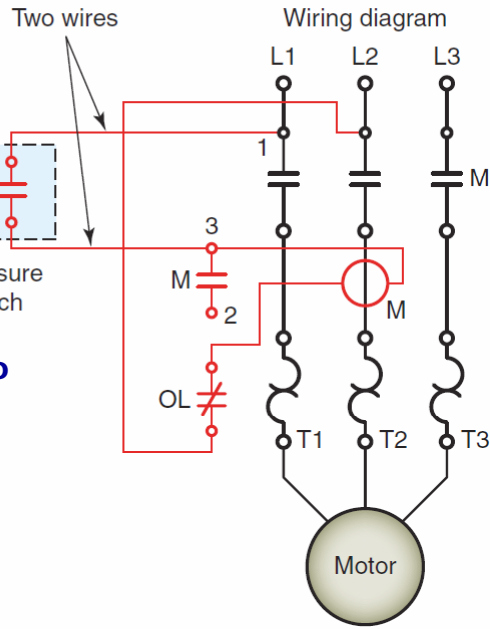Two-wire control circuits are designed to start on stop a motor when a remote control device such as a thermostat or level switch is activated or deactivated.



© 2010, The McGraw-Hill Companies, Inc.

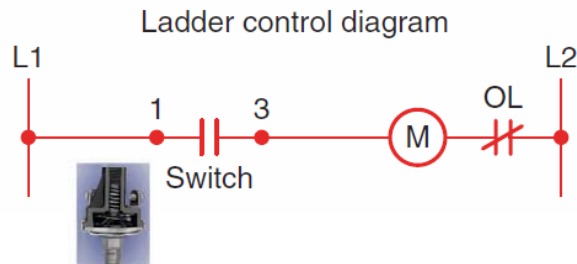The starter operates automatically in response to the state of the control device without the assistance of an operator.



The two-wire circuit provide *low-voltage release but not low-voltage protection*. If the motor is stopped by a power interruption, the starter deenergizes (low-voltage release), but also reenergizes if the control device remains closed when the circuit has power restored.

© 2010, The McGraw-Hill Companies, Inc.


Two-wire control circuits are used to automatically operate machinery where the automatic restarting characteristic is desirable and there is no danger of persons being injured if the equipment should suddenly restart after a power failure.



**Typical application
– well pump**

© 2010, The McGraw-Hill Companies, Inc.

Simulated Two-Wire Control Circuit

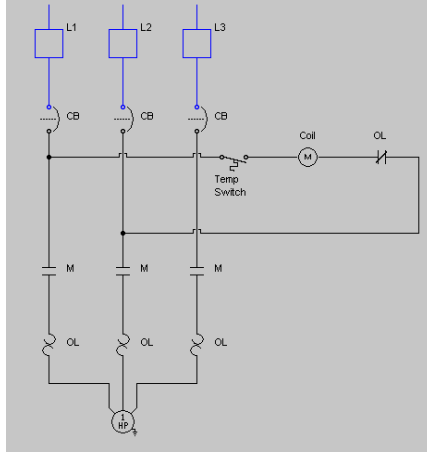


© 2010, The McGraw-Hill Companies, Inc.

THREE-WIRE CONTROL CIRCUIT

© 2010, The McGraw-Hill Companies, Inc.


Three-Wire Control Circuit

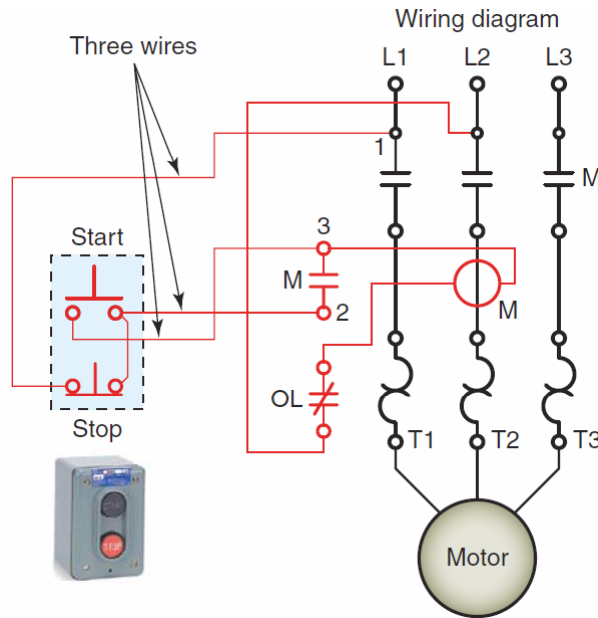Three-wire control provides both **low-voltage release and low-voltage protection**. This means that the starter will drop out when there is a voltage failure, but it will not pick up automatically when voltage returns.





© 2010, The McGraw-Hill Companies, Inc.

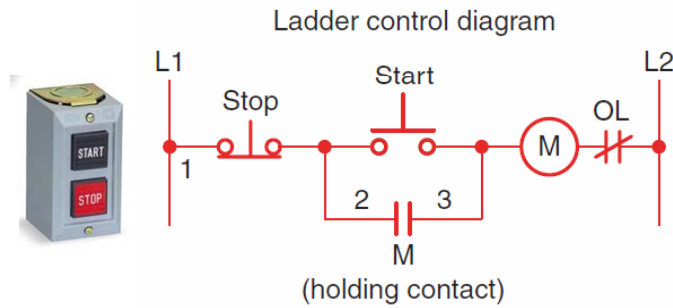One of the most common examples of a three-wire control circuit is the start/stop, pushbutton control station.




The circuit uses a normally closed stop pushbutton wired in series with the parallel combination consisting of normally open start pushbutton and normally open holding contact (M).

© 2010, The McGraw-Hill Companies, Inc.

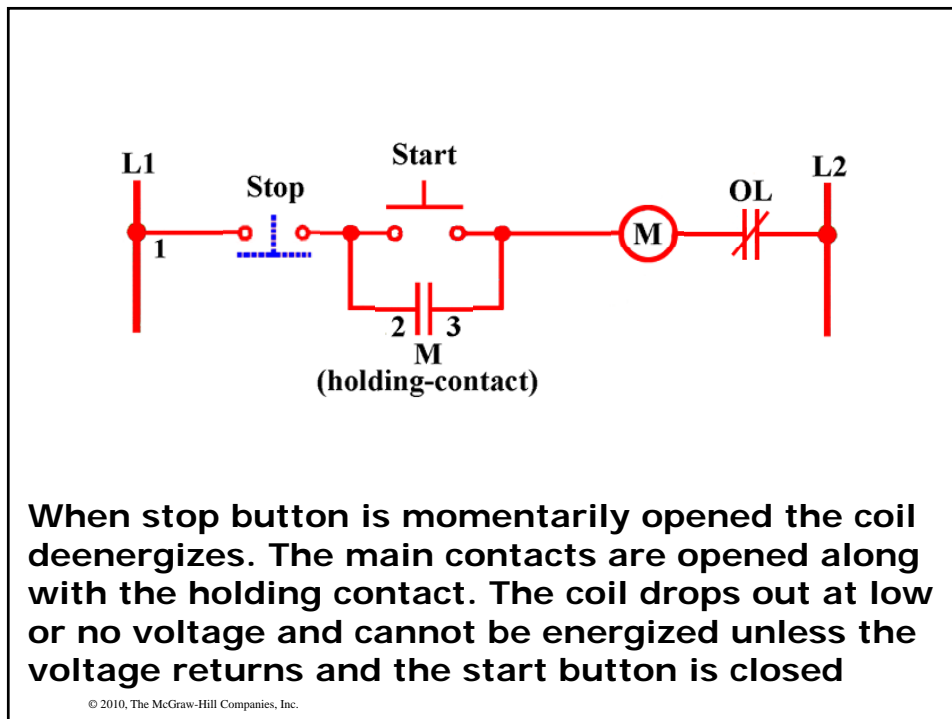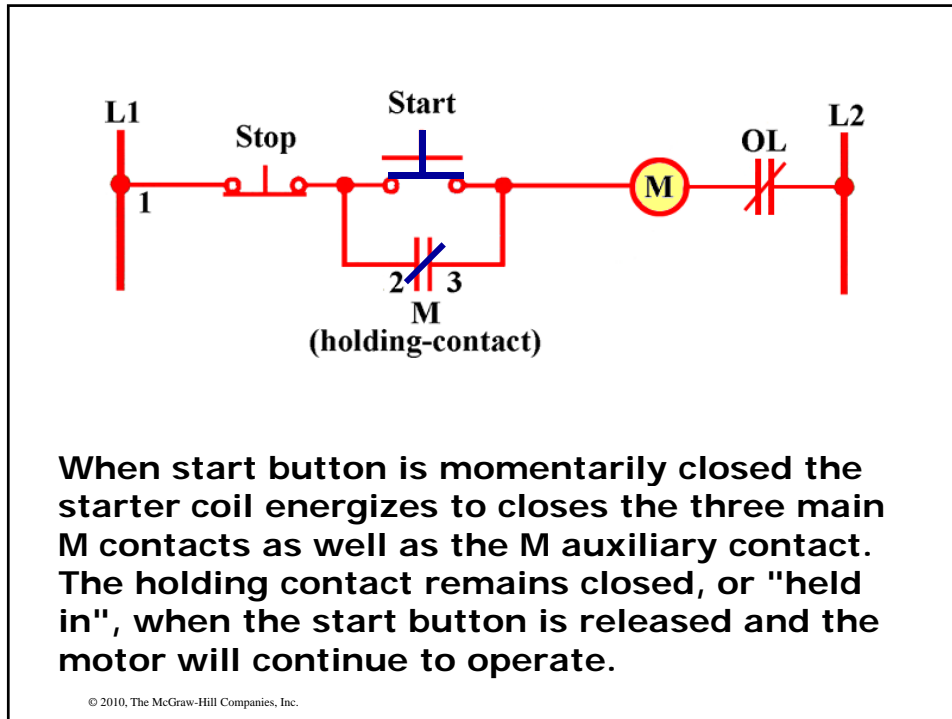


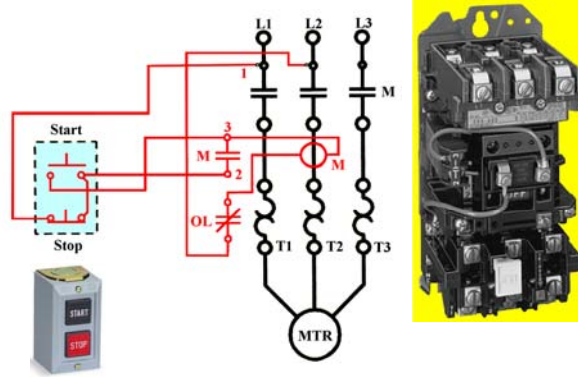In the event of a power failure the maintaining circuit is designed to protect against automatic restarting when the power returns. This type of protection must be used where accidents or damage might result from unexpected starts.



© 2010, The McGraw-Hill Companies, Inc.

Simulated Three-Wire Control Circuit

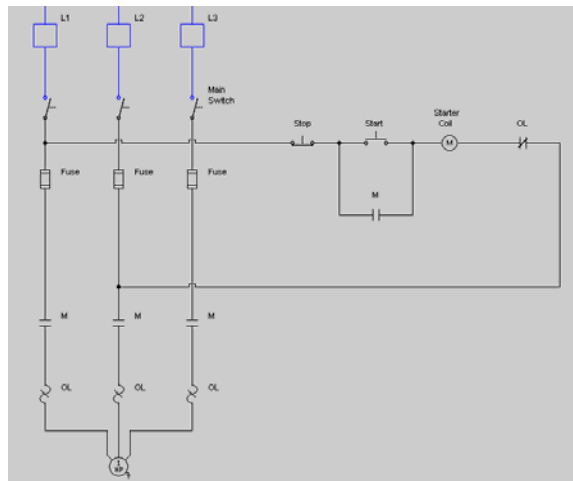

© 2010, The McGraw-Hill Companies, Inc.