


Chapter 8


Motor Control Circuits

© 2010, The McGraw-Hill Companies, Inc.

Understanding the rules detailed in the **National Electrical Code is critical to the proper installation of motor control circuits.**



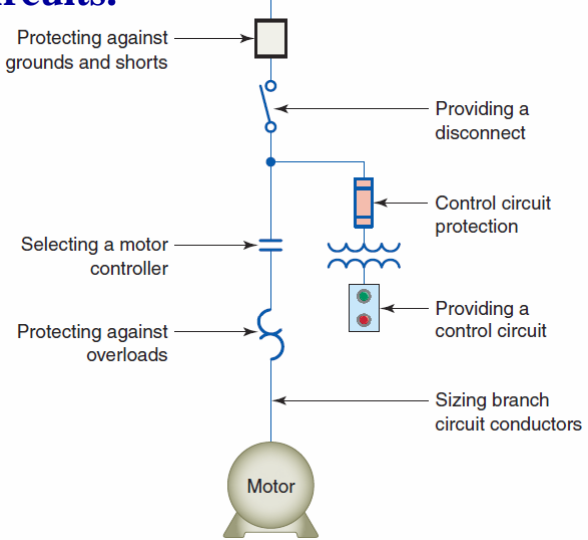Article 430 of the NEC covers application and installation of motor circuits.



Protecting against grounds and shorts

Providing a disconnect

Control circuit protection

Providing a control circuit

Sizing branch circuit conductors


Protecting against overloads

Selecting a motor controller

Motor


© 2010, The McGraw-Hill Companies, Inc.

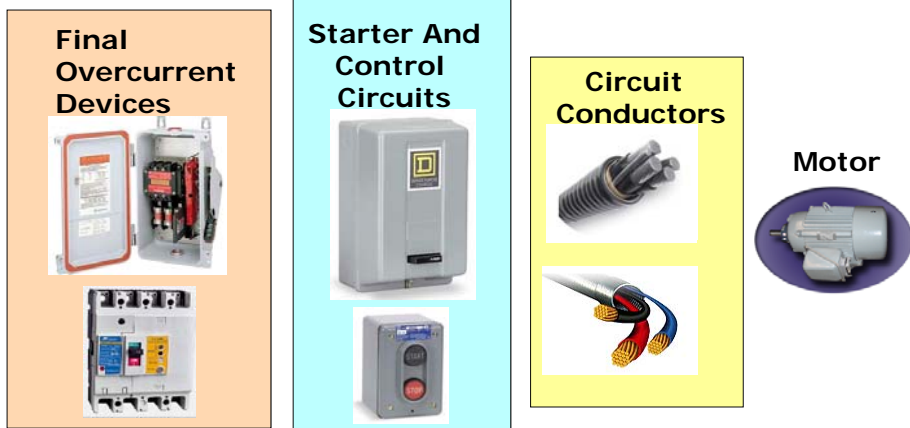A motor branch-circuit includes the final overcurrent device, the motor starter and associated control circuits, circuit conductors and the motor.



© 2010, The McGraw-Hill Companies, Inc.

Motor Branch Circuit Sections

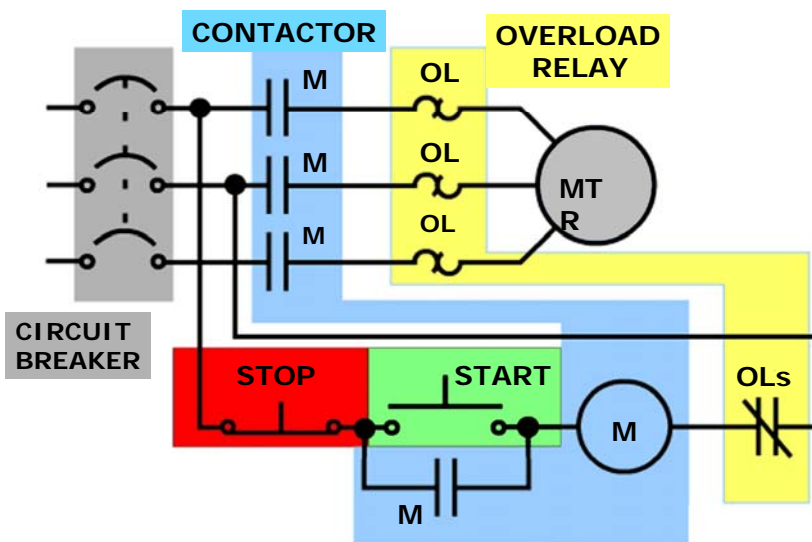

© 2010, The McGraw-Hill Companies, Inc.

The full-load current rating shown on the motor nameplate *is not* permitted to be used to determine the ampacity of the

- conductors
- switches
- motor branch-circuit short-circuit and ground-fault protection.





The reasons are:

- ❑ The supply voltage normally varies from the voltage rating of the motor, and the current varies with the voltage applied.
- ❑ The actual full-load current rating for motors of the same horsepower may vary, and requiring the use of NEC tables ensures that if a motor must be replaced, this can be safely done without having to make changes to other component parts of the circuit.

© 2010, The McGraw-Hill Companies, Inc.

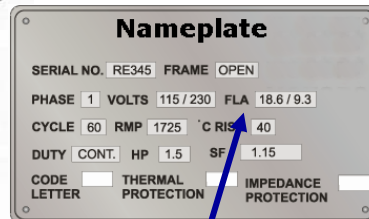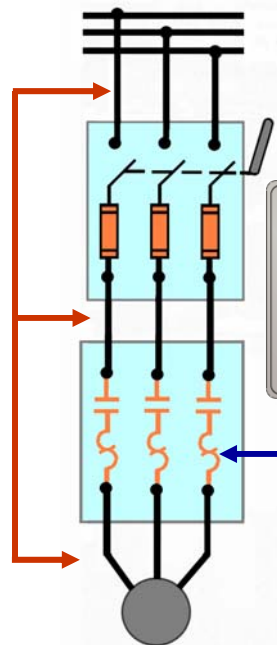Conductor ampacity must be determined by *NEC Tables 430-247 through 430-250* and are based upon the motor nameplate horsepower rating and voltage.




Overload protection, however, is based on the marked motor nameplate rating.

© 2010, The McGraw-Hill Companies, Inc.

BRANCH CIRCUIT MOTOR PROTECTION

© 2010, The McGraw-Hill Companies, Inc.

Motor Branch Circuit Protection

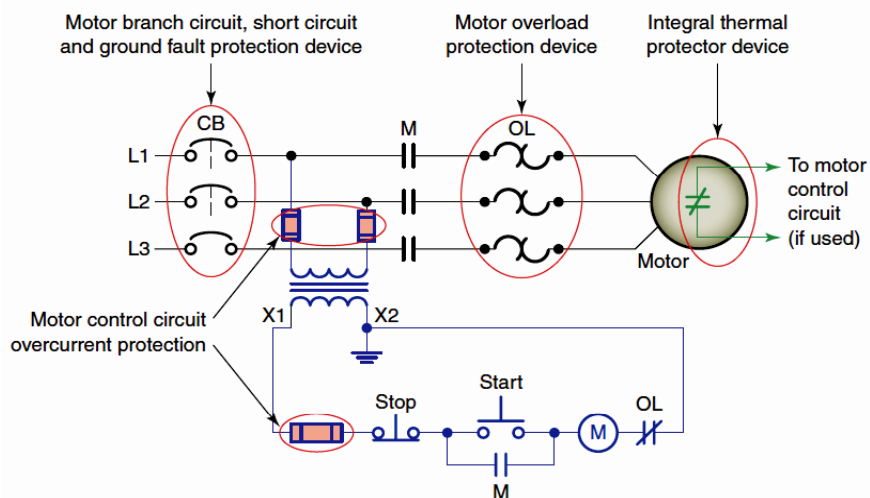

This arrangement makes motor protection calculations different from those used for other types of loads.


© 2010, The McGraw-Hill Companies, Inc.

Time-delay fuses provide overload and short circuit protection usually allowing **five times** the rated current for up to **ten seconds** to allow motors to start.



Nontime-delay fuses provide short circuit protection usually allowing about **five times** of their rating for approximately **one-fourth second**, after which the current-carrying element melts.

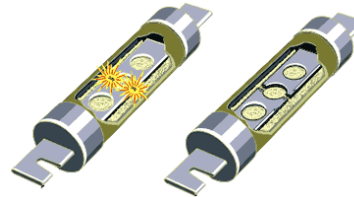The amount of time it takes for a fuse to open is known as the **clearing time**. Fuses have an **inverse time characteristic**. The greater the overcurrent, the less the clearing time.




© 2010, The McGraw-Hill Companies, Inc.

A motor overload condition is caused by excessive load applied to the motor shaft.

For example, when using a saw, if the board is damp or the cut is too deep, the motor may become overloaded and slow down. The current flow in the windings will increase and heat the motor beyond its design temperature.




Overloaded Motor

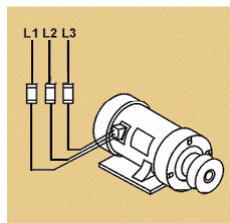

Fuses are large enough to allow starting current


© 2010, The McGraw-Hill Companies, Inc.

Fuses do not blow

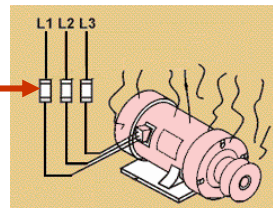


Additional overload protection required

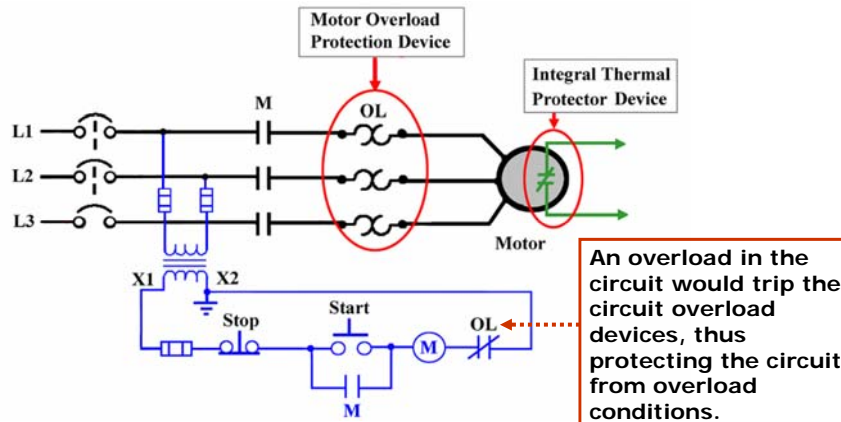Motors are required to have overload protection, either **within the motor itself** or somewhere **in close proximity** to the line side of the motor. This overload protection is actually protecting the motor, the conductors, and much of the circuit ahead of the overloads.



© 2010, The McGraw-Hill Companies, Inc.

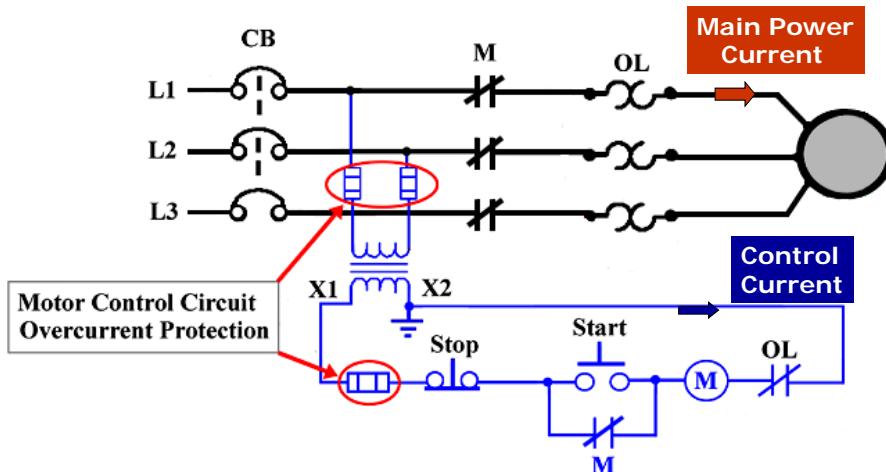Motor **control circuits** carry the current that controls the operation of the controller, but do not carry the main power current to the motor.




© 2010, The McGraw-Hill Companies, Inc.

SELECTING A MOTOR CONTROLLER


© 2010, The McGraw-Hill Companies, Inc.

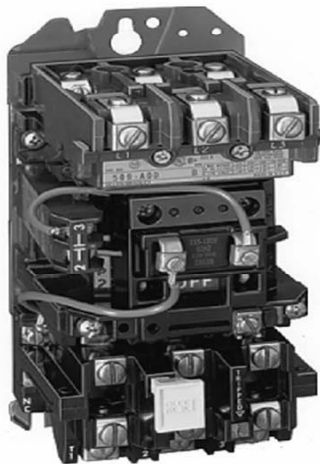*A motor controller is any device that is used to **directly start and stop** an electric motor by closing and opening the main power current to the motor.*



© 2010, The McGraw-Hill Companies, Inc.

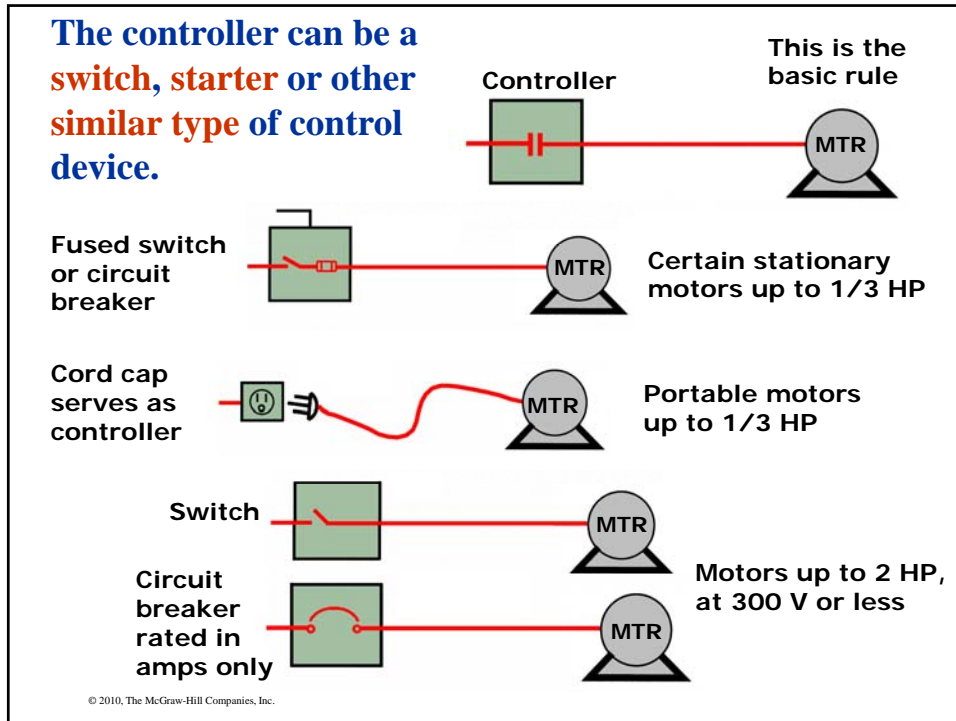The **magnetic starter** consisting of a contactor and overload relay is considered to be a controller.



**DISCONNECTING
MEANS FOR
MOTOR AND
CONTROLLER**

© 2010, The McGraw-Hill Companies, Inc.

The ability to safely work on a motor, a motor controller or any motor-driven machinery starts with being able to **turn the power off** to the motor and its related equipment.


The Code requires that a means (a **motor-circuit switch rated in HP or a circuit breaker**) must be provided in each motor circuit to **disconnect** both the motor and its controller from **all ungrounded supply conductors**.



HP Rated Switch

© 2010, The McGraw-Hill Companies, Inc.

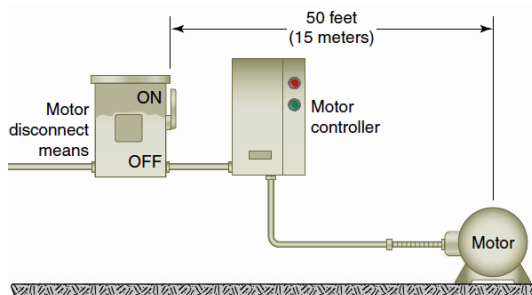The NEC requires that for motor circuits rated 600 volts or less, the disconnecting means must be located in **sight from the controller, motor and the driven machinery location**.



In sight from is defined as being visible and not more than **50 ft (15m)**


One Exception to this basic requirement is that a disconnect does not have to be within sight if the required disconnect ahead of the motor controller is capable of being **locked in the OPEN position**.

© 2010, The McGraw-Hill Companies, Inc.

PROVIDING A CONTROL CIRCUIT

© 2010, The McGraw-Hill Companies, Inc.

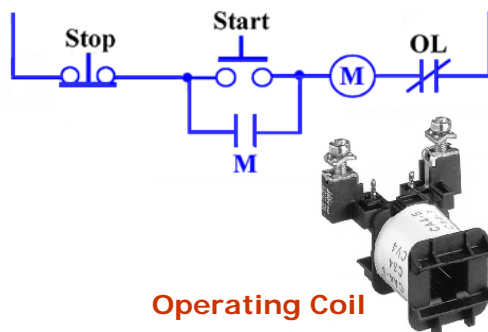A **motor control circuit** carries electrical signals directing the **action of the controller** but does not carry the main power circuit.



The control circuit commonly has as its load device the **operating coil** of a magnetic motor starter, a magnetic contactor, or a relay.

© 2010, The McGraw-Hill Companies, Inc.

Control circuits associated with motor controls can be complex and vary greatly with application.




Elements of a control circuit include:

- Conductors and raceways
- Contactor operating coil
- Source of energy supply to the circuit
- Overcurrent protection devices
- All switching devices that govern energization of the operating coil.

© 2010, The McGraw-Hill Companies, Inc.

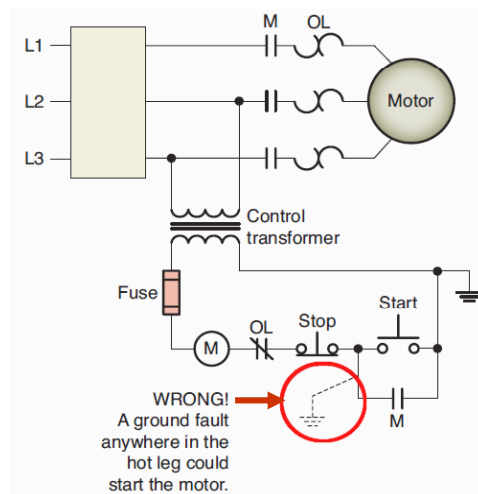Where one side of the motor control circuit is grounded, the control circuit must prevent the motor from being started due to a ground fault in the control circuit wiring.




© 2010, The McGraw-Hill Companies, Inc.

**WRONGLY
DESIGNED
CONTROL CIRCUIT**

If one side of the start button is in the ground leg of the circuit, as shown, a ground fault on the coil side of the start button can short – circuit the start circuit and start the motor.

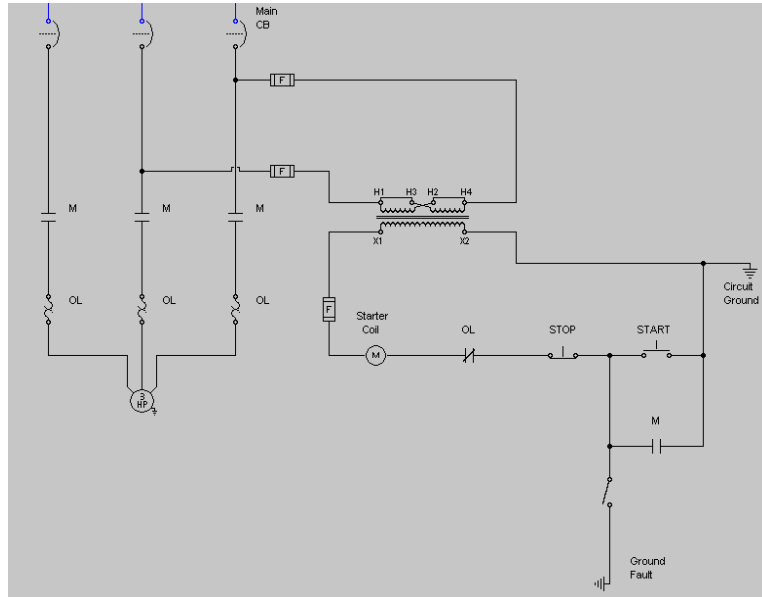
Simulated **Wrongly Designed** Control Circuit



© 2010, The McGraw-Hill Companies, Inc.


CORRECTLY DESIGNED CONTROL CIRCUIT

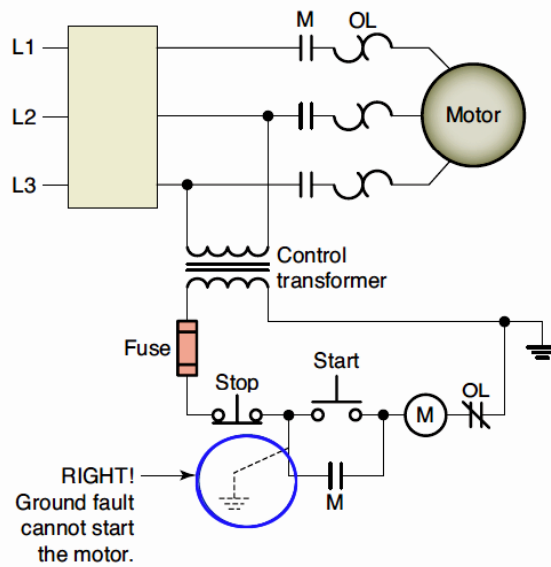By switching the hot leg, as shown, the starting of the motor due to an accidental ground fault can be effectively eliminated.



© 2010, The McGraw-Hill Companies, Inc.

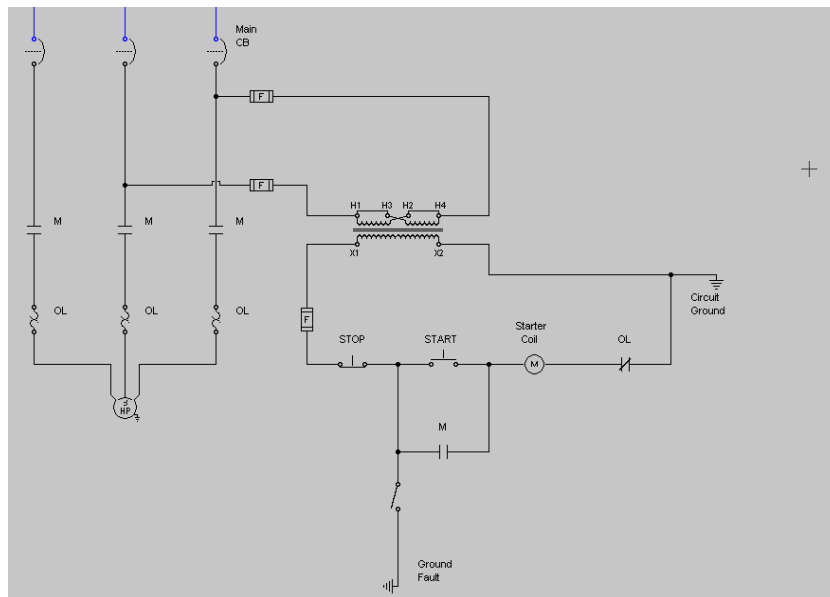Simulated **Correctly Designed** Control Circuit



© 2010, The McGraw-Hill Companies, Inc.

➤ Where a transformer is used to obtain a reduced voltage for the motor control circuit and the transformer is located within the motor controller enclosure, the transformer must be **connected to the load side of the motor control circuit** disconnecting means. The control transformer must be protected in accordance with **NEC Article 430.72(C)**




© 2010, The McGraw-Hill Companies, Inc.

FULL VOLTAGE STARTING OF AC INDUCTION MOTORS

© 2010, The McGraw-Hill Companies, Inc.

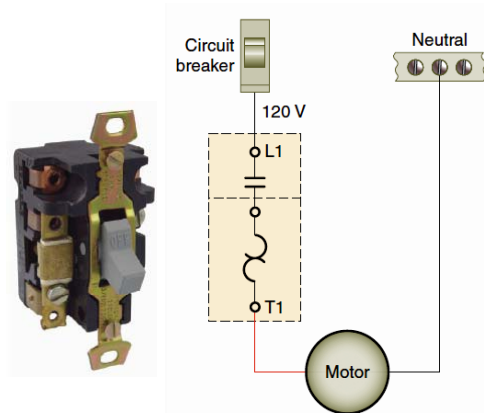A full voltage, or across-the-line, starter is designed to apply full line voltage to the motor upon starting.



**Fractional horsepower manual
across-the-line starter**



© 2010, The McGraw-Hill Companies, Inc.

➤ Uses an ON/OFF snap-action switch with overload protection.

➤ When started the motor is connected directly across the line and in series with the starter contact and overload device.

➤ When an overload is sensed, the starter contacts open and cannot be reclosed until the overload relay is reset manually.

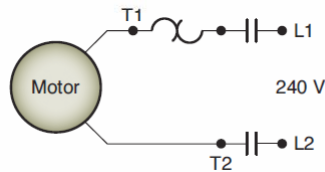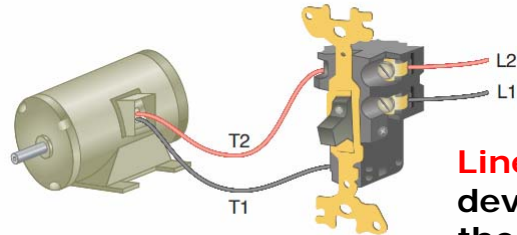
Double-pole manual motor starter with a single overload heater to protect the motor windings.



© 2010, The McGraw-Hill Companies, Inc.

Line rated control devices such as thermostats, float switches and relays are used to connect and disconnect the motor when automatic operation is desired.

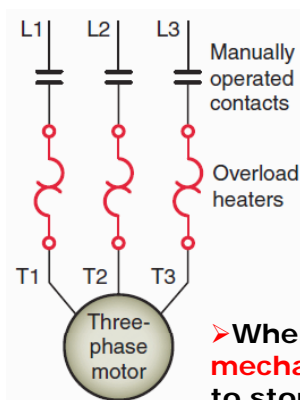A three-pole manual starter provides three overload heaters to protect the motor windings.




➤ This starter is operated by pushing a button on the starter enclosure cover that **mechanically** operates the starter.

➤ When an overload relay trips, the starter **mechanism unlatches**, opening the contacts to stop the motor.

➤ The contacts cannot be reclosed until the starter mechanism has been reset by pressing the STOP button; first, however, the thermal unit needs time to **cool**.


© 2010, The McGraw-Hill Companies, Inc.

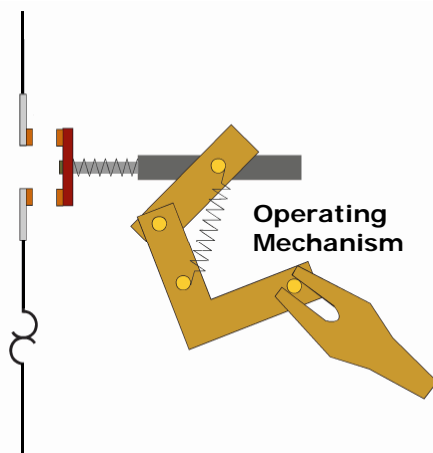The power circuit contacts of manual motor starters are unaffected by the loss of voltage, so consequently will **remain closed** when the supply **voltage fails**.



➤ If the supply voltage fails, the motor will stop and **restart automatically** when the supply voltage is restored (**no voltage release**).

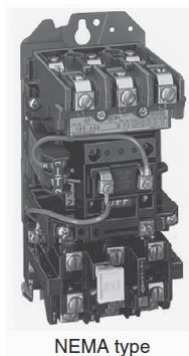➤ Manual starters must be mounted near the motor that is being controlled. Remote control operation is not possible as it would be with a magnetic starter.





The **magnetic starter** contacts are closed by energizing a **holding coil**.




➤ This enables the use of **automatic** and **remote** control of the motor.

➤ Pushbutton stations are mounted nearby, but automatic control pilot devices can be mounted almost anywhere on the machine.

© 2010, The McGraw-Hill Companies, Inc.

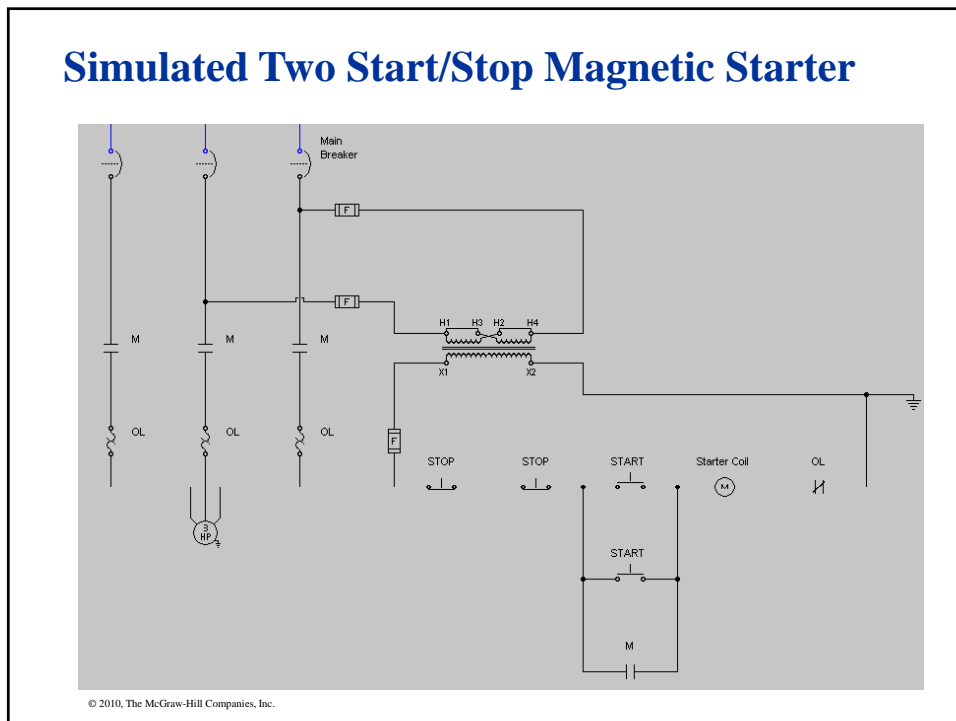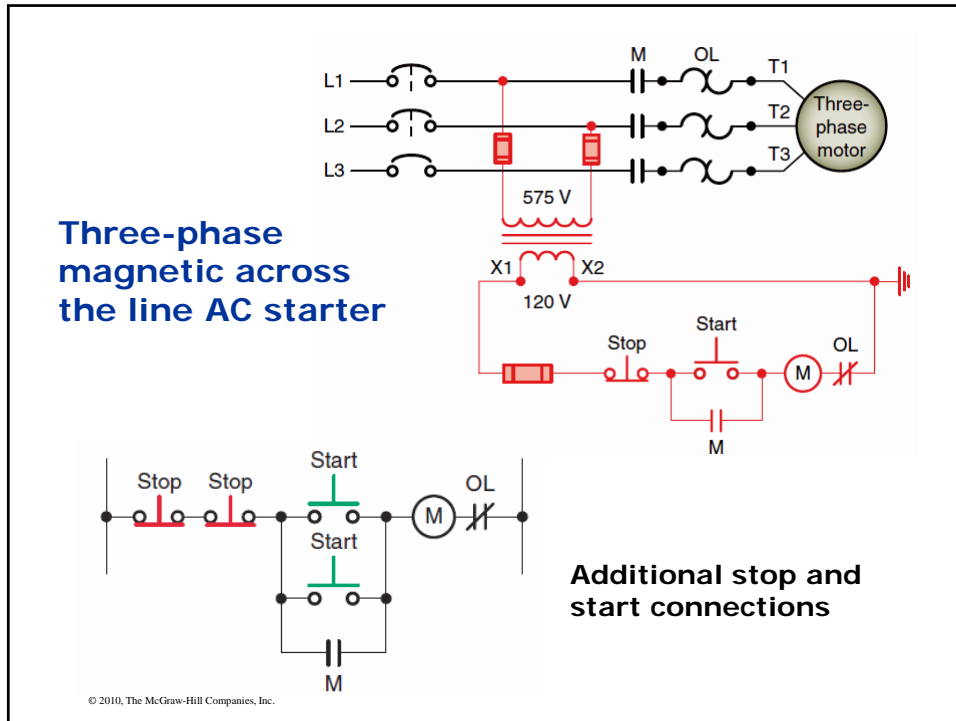

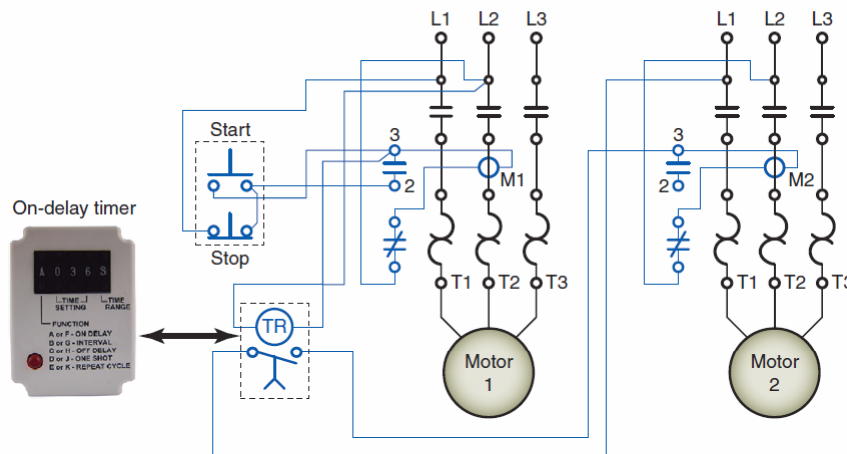
Circuit used to start two motors at full line voltage.



Power and control circuit wiring

© 2010, The McGraw-Hill Companies, Inc.

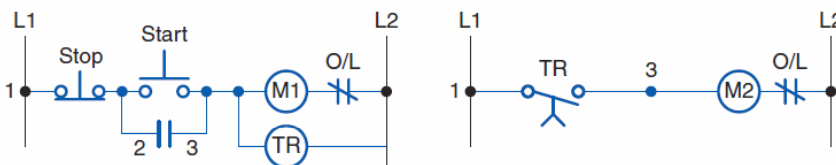
Circuit used to start two motors at full line voltage.



- The first motor is started by pressing the start button connected in a three-wire control configuration to motor starter M1.
- Power is applied to both Motor 1 and on-delay timer coil TR.
- After the preset time, normally open timer contacts TR close to energize starter coil M2 and the second motor starts.
- Both motors will stop by pressing the stop button.

© 2010, The McGraw-Hill Companies, Inc.

Simulated two motor starting circuit.

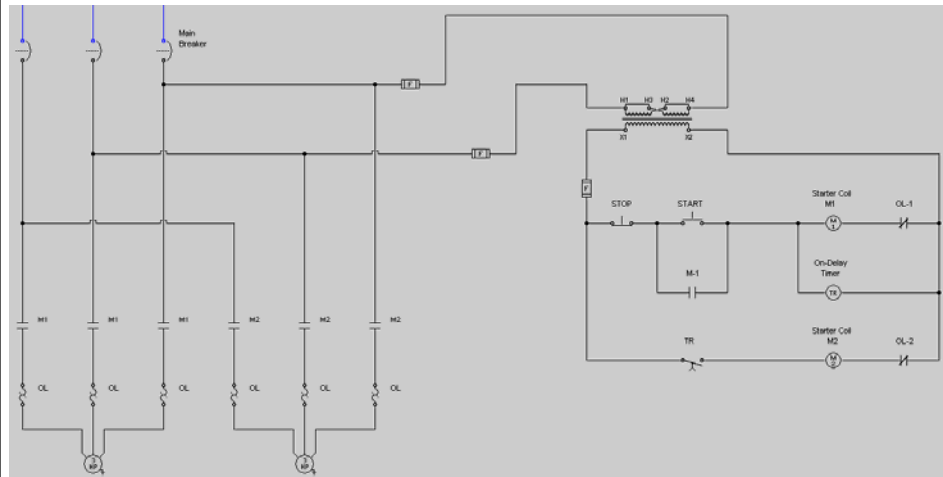

© 2010, The McGraw-Hill Companies, Inc.

REDUCED VOLTAGE STARTING OF INDUCTION MOTORS

© 2010, The McGraw-Hill Companies, Inc.


Reduced voltage starters limit line voltage disturbances and lower excessive starting torque



- The large starting in-rush current of a large size motor could cause line voltage dips and brownouts.
- In addition to high starting currents, the motor also produces starting torques that are higher than full-load torque. In many applications this starting torque can cause excessive mechanical, damage such as belt, chain, or coupling breakage.
- When a reduced voltage is applied to motor at rest, both the current drawn by the motor and the torque produced by the motor are reduced.

© 2010, The McGraw-Hill Companies, Inc.

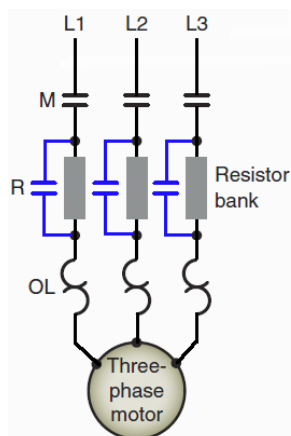
Reduced voltage is obtained in the primary resistance starter by means of resistances that are connected in series with each motor stator lead during the starting period.




➤ The voltage drop in the resistors produces a reduced voltage at the motor terminals.

➤ After a preset time period the "R" contacts close to short circuit the starting resistors and apply full line voltage to the motor.


© 2010, The McGraw-Hill Companies, Inc.

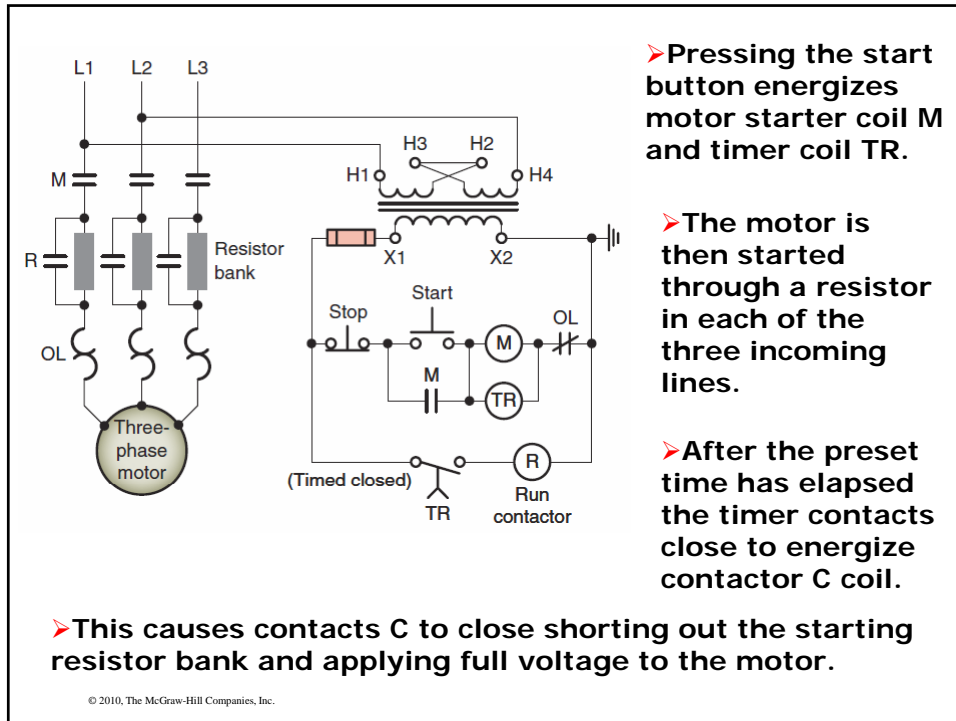

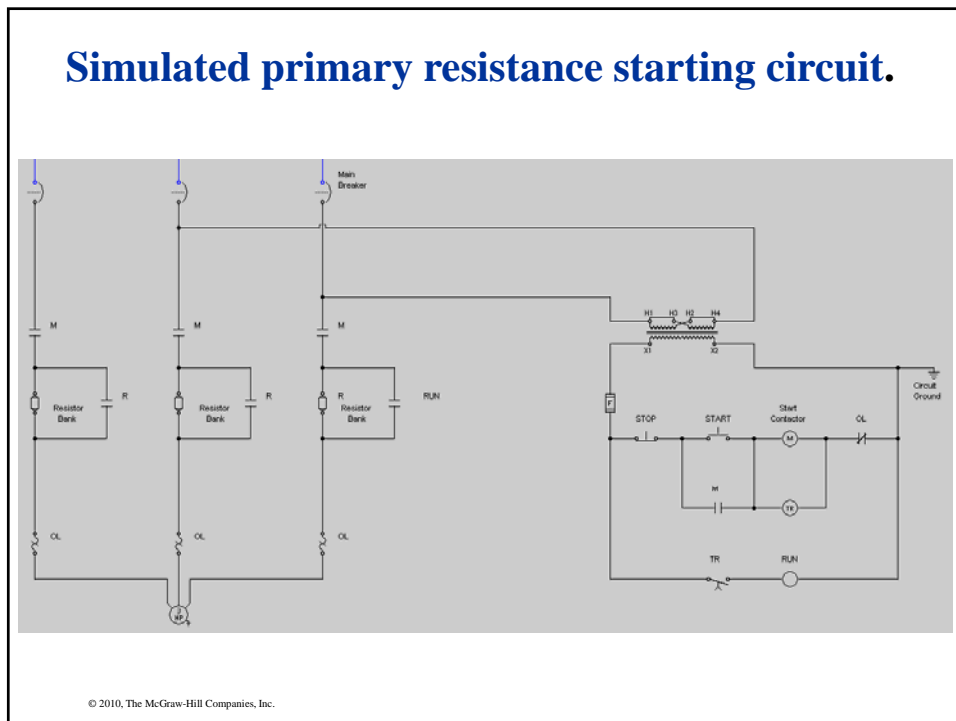Simulated primary resistance starting circuit.



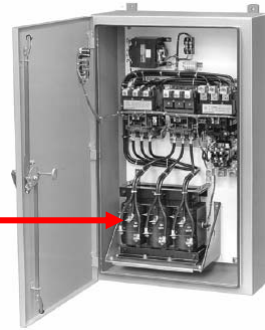
The autotransformer starter uses a step-down autotransformer to reduce the line voltage.



➤ **Multiple taps** on the transformer permit the voltage, current, and torque to be adjusted to satisfy many different starting conditions.

➤ In **closed transition** starting, the motor is never disconnected from the line source during acceleration.

© 2010, The McGraw-Hill Companies, Inc.

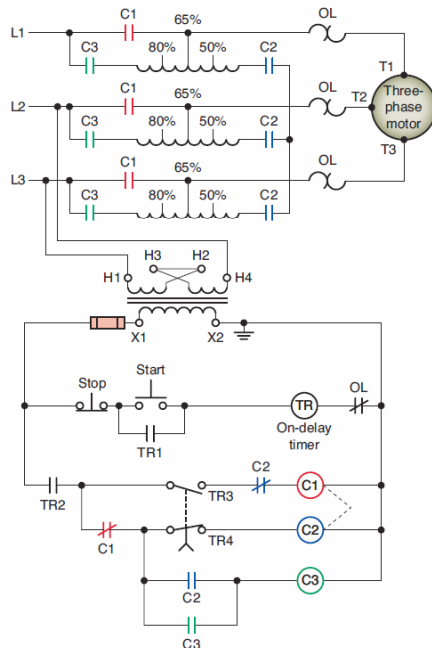

➤ On starting timer coil TR and contactor coils C2 and C3 are energized.

➤ Main contacts C2 and C3 close and the motor is connected through the transformers taps to the power line.


➤ After the starting period has elapsed TR timed contacts operate to de-energize contactors C2 and C3 and energize contactor C1, resulting in the connection of the motor to full line voltage.

© 2010, The McGraw-Hill Companies, Inc.


The **Wye-Delta** starter connects the motor windings first in Wye during the starting period and then in Delta after the motor has accelerated.



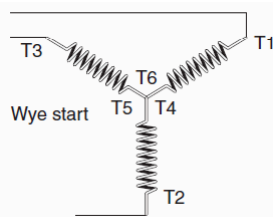
Wye-delta starters can only be used with three-phase AC motors where all **six leads** of the stator windings are available.



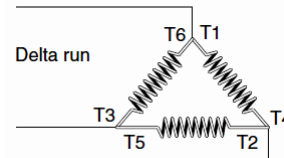When **wye** connected the motor starts with a significantly lower current than when **delta** connected.



© 2010, The McGraw-Hill Companies, Inc.

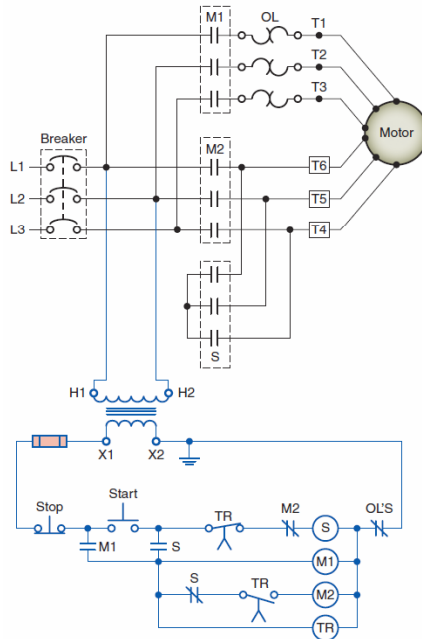


➤ On starting coils **S**, **M1** and **TR** are energized connecting the motor winding in a **wye** configuration

➤ After the time delay period has elapsed, the **TR** contacts change state to **de-energize** contactor coil **S** and energize contactor coil **M2**.

➤ The motor then continues to run with the motor connected in a **delta** arrangement.


© 2010, The McGraw-Hill Companies, Inc.

Simulated Wye-Delta Starter

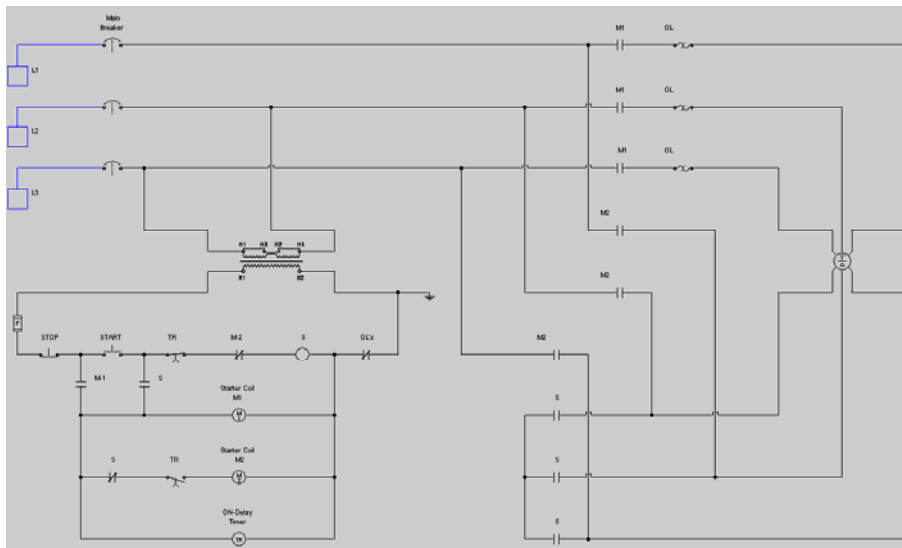

© 2010, The McGraw-Hill Companies, Inc.

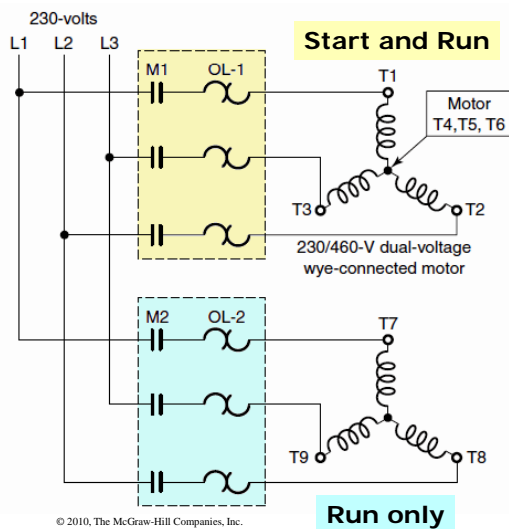Part-winding starters are used on induction motors wound for dual voltage operation (e.g. 230/460 V)



© 2010, The McGraw-Hill Companies, Inc.

Power is applied to **part of the motor windings** on startup and then connects the remaining coils for normal speed.

230/460 V motor operated @ 230 V

© 2010, The McGraw-Hill Companies, Inc.

- These motors have two sets of windings connected in **parallel** for low-voltage operation and in **series** for high-voltage operation.
- When used on the **lower voltage**, they can be started by first energizing only one winding, limiting starting current and torque to approximately one-half of the full voltage values.
- The second winding is then connected in **parallel**, once the motor nears operating speed.
- Since one set of windings has **higher impedance** than the two connected in parallel, less inrush current flows to the motor on startup.

- On starting coils **M1** and **TR1** are energized.
- **M1 contacts close** immediately starting the motor at reduced current and torque through one-half of the wye windings.
- After the preset time has elapsed the **timer contacts close** to energize starter coil **M2** applying voltage to the second set of wye windings.

230-volts
L1 L2 L3

M1 OL-1
M2 OL-2

T1 T2 T3 T7 T8 T9

Motor T4, T5, T6

230/460-V dual-voltage wye-connected motor

➤ It is of utmost importance to connect the motor terminals (T1, T2, T3, T7, T8 and T9) to the proper terminals on the motor starter.

➤ When motor winding T7- T8- T9 is connected, it must produce the same rotation.


If by chance an error has been made, and T8 and T9 were interchanged, the second winding will attempt to change the rotation of the motor. Extremely high current will then flow, damaging the equipment.

© 2010, The McGraw-Hill Companies, Inc.

Electronic soft-starters limit motor starting current and torque by ramping (gradually increasing) the voltage applied to the motor during the selected starting time.

Current limit is used when it is necessary to limit the maximum starting current and is usually adjustable.

© 2010, The McGraw-Hill Companies, Inc.

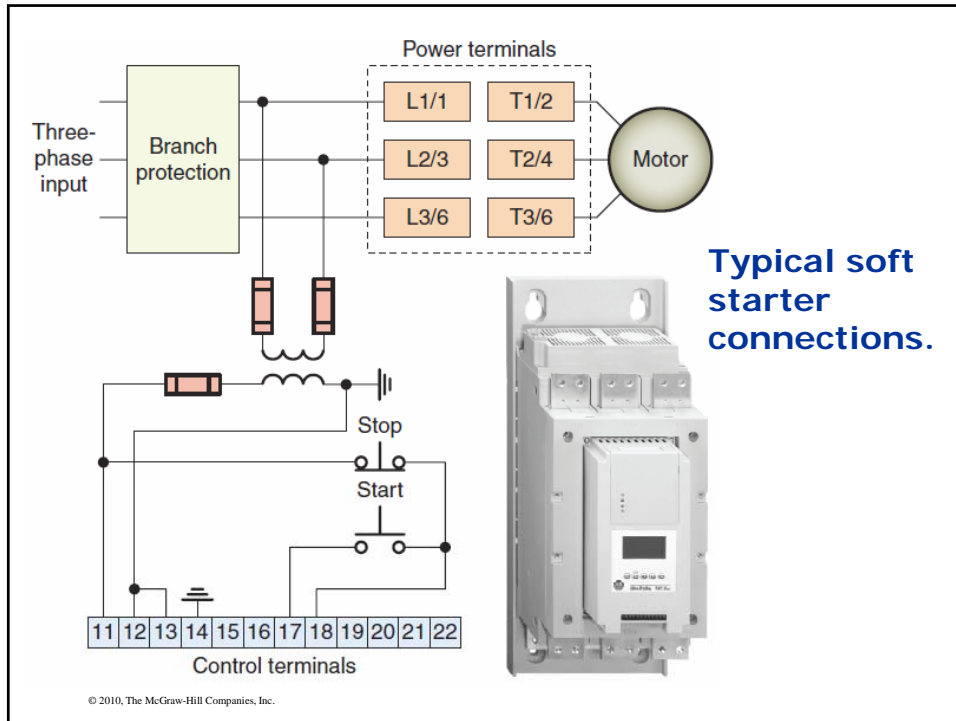


DC MOTOR STARTING

One major difference between **AC and DC** starters are the electrical and mechanical requirements necessary for **suppressing the arcs** created in opening and closing contacts under load.

To combat **prolonged arcing in DC circuits**, the contactor switching mechanism is constructed so that the contacts will separate rapidly and with enough air gap to extinguish the arc as soon as possible on opening.




© 2010, The McGraw-Hill Companies, Inc.

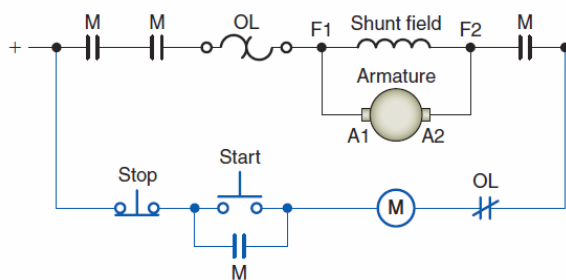


Across-the-line DC motor starter

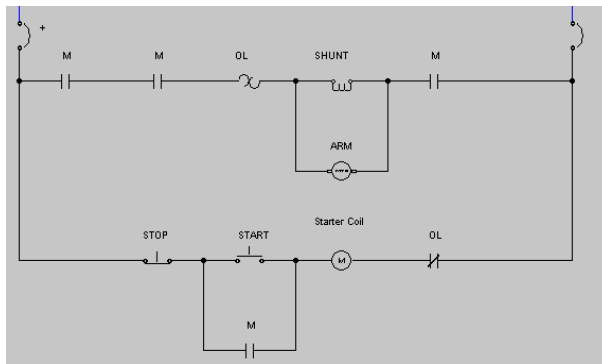To help extinguish the arc, the starter is equipped with **three power contacts connected in series**.



© 2010, The McGraw-Hill Companies, Inc.

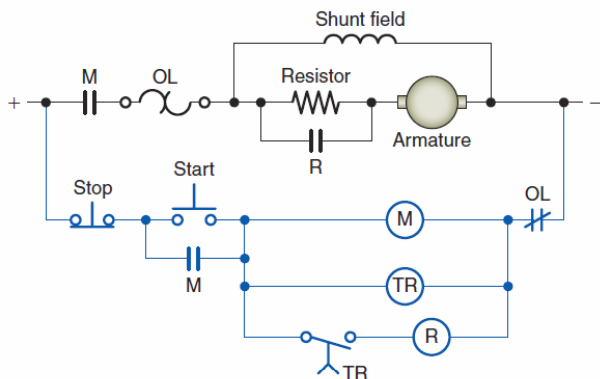Definite-time reduced voltage DC motor starter.




➤ When the M contact closes, full line voltage is applied to the shunt field while the resistor is connected in series with the armature.

➤ Following a preset time period, the contactor R closes, bypassing the resistor, allowing the motor to operate at base speed.

➤ This gives the motor smooth torque without creating a large surge of current.

© 2010, The McGraw-Hill Companies, Inc.

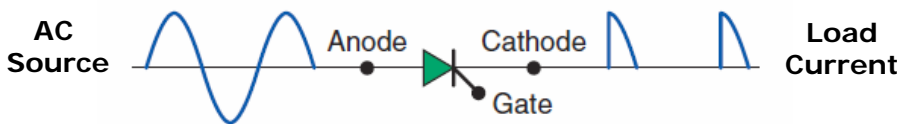Variable voltage acceleration of a DC shunt motor can be obtained by using an SCR (Silicon Controlled Rectifier) armature voltage controller.




An SCR is a semiconductor device that has three elements: anode, cathode, and gate.



The SCR provides a useful method of converting AC voltage to variable DC voltage.

© 2010, The McGraw-Hill Companies, Inc.

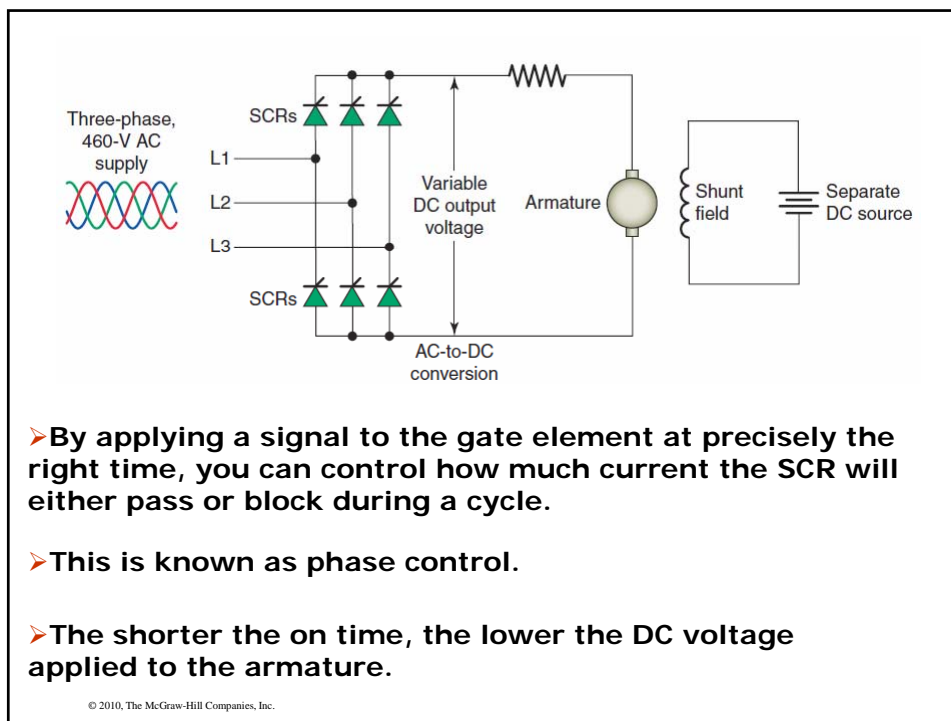

REVERSING OF AC INDUCTION MOTORS

REVERSING THREE-PHASE INDUCTION MOTOR STARTER

© 2010, The McGraw-Hill Companies, Inc.


Interchanging any **two leads** to a three-phase induction motor will cause it to run in the **reverse direction**.



The industry standard is to interchange phase A (Line 1) and phase C (Line 3), while **phase B (Line 2) remains the same**.

© 2010, The McGraw-Hill Companies, Inc.

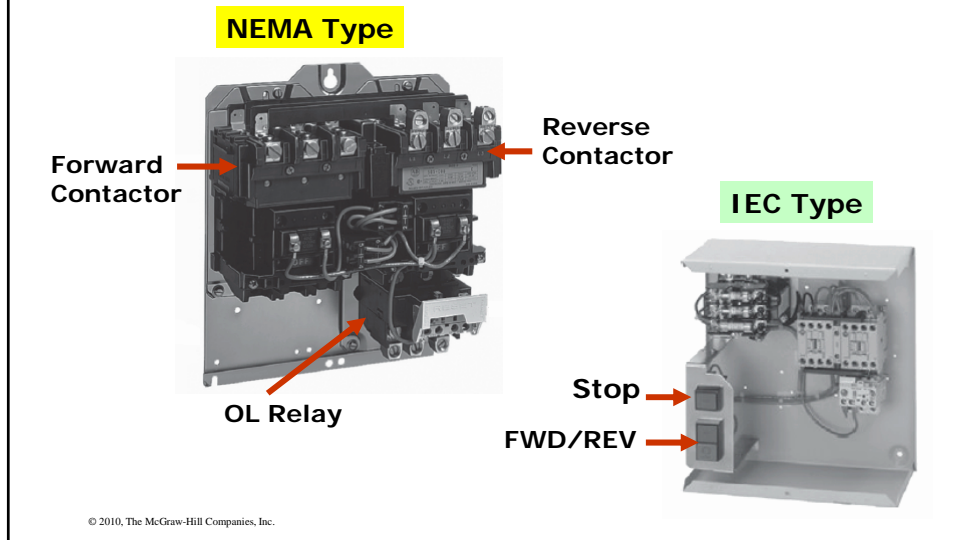Reversing starters are used to automatically accomplish phase reversal.




Power circuit of a magnetic full voltage three-phase reversing motor starter

➤ Uses **two** three-pole contactors with a **single overload** relay assembly.

➤ The power circuits of the two contactors are interconnected.


➤ Contacts **F** connect L1, L2, and L3 to motor terminals T1, T2, and T3, respectively.

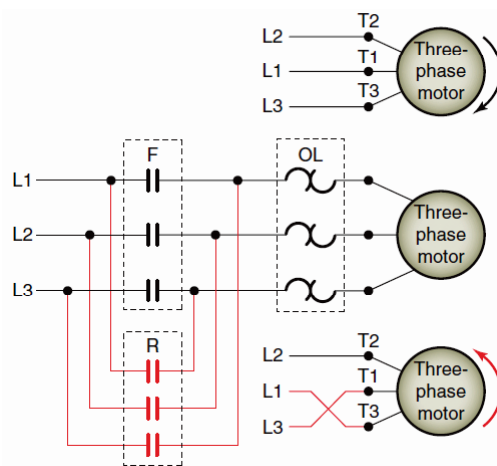➤ Contacts **R** connect L1 to motor terminal T3 and connect L3 to motor terminal T1, causing the motor to reverse direction.



© 2010, The McGraw-Hill Companies, Inc.

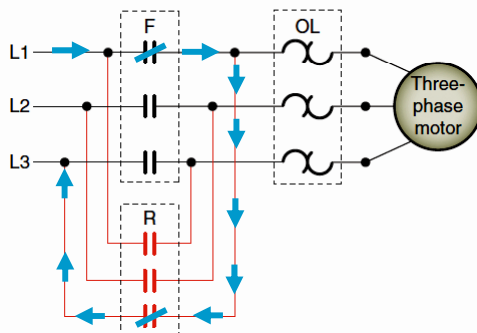
When reversing the motor, it is vital that the forward and reverse contactors **not** be energized at the same time.



Activating both contactors would cause a **short circuit** since two of the line conductors are reversed on one contactor.

© 2010, The McGraw-Hill Companies, Inc.

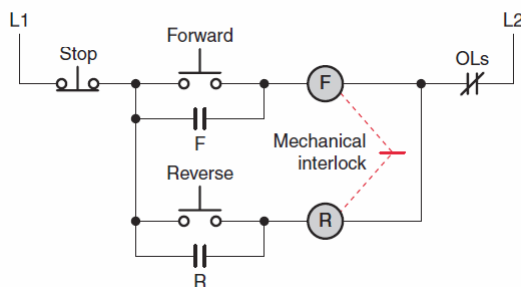
Both **mechanical** and **electrical** interlocks are used to prevent the forward and reverse contactors from being activated at the same time.



- Mechanical interlocking uses a system of levers to prevent both contactors from being engaged at the same time.
- The broken line indicates that the coils F and R cannot close contacts simultaneously because of the mechanical interlocking action of the device.


© 2010, The McGraw-Hill Companies, Inc.

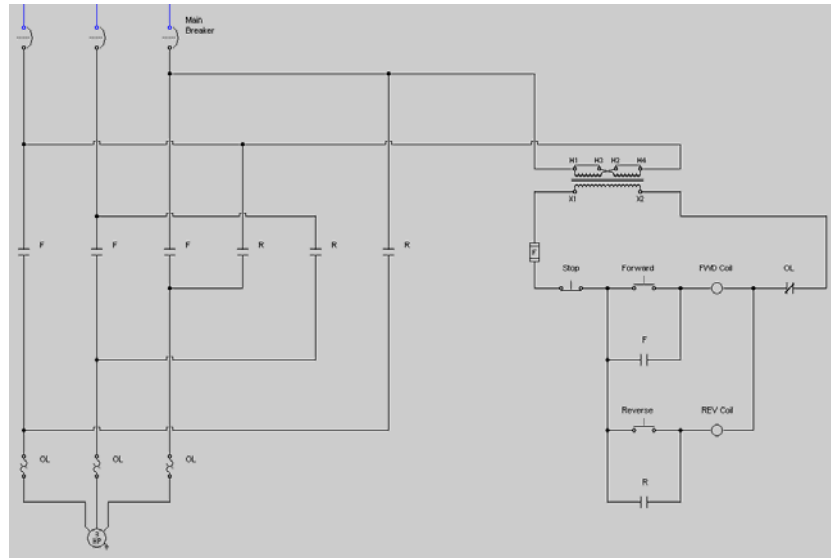Simulated Reversing Starter With **No Interlocking**




© 2010, The McGraw-Hill Companies, Inc.

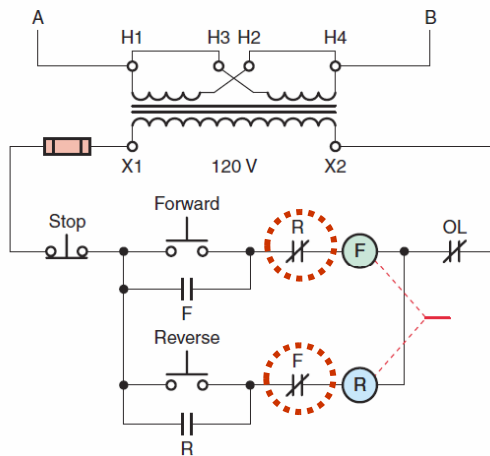Mechanical interlocks have been known to fail and for this reason additional **electrical interlocking is used for added protection.**




© 2010, The McGraw-Hill Companies, Inc.


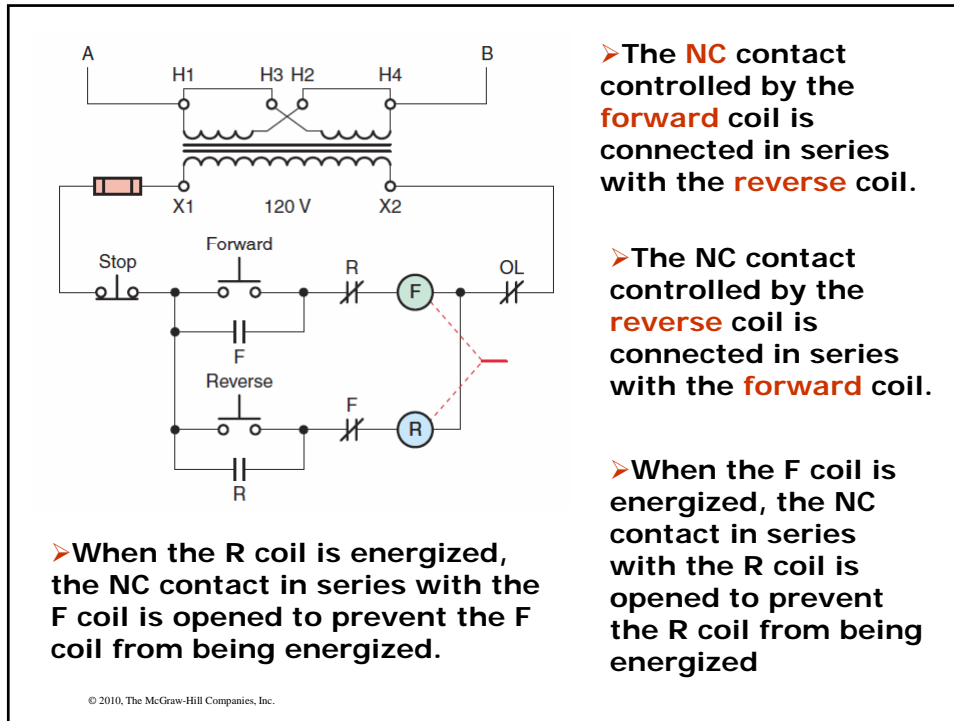
Most reversing starters utilize **auxiliary contacts operated by the forward and reverse coils to provide electrical interlocking.**



Simulated Auxiliary Contact Interlocking

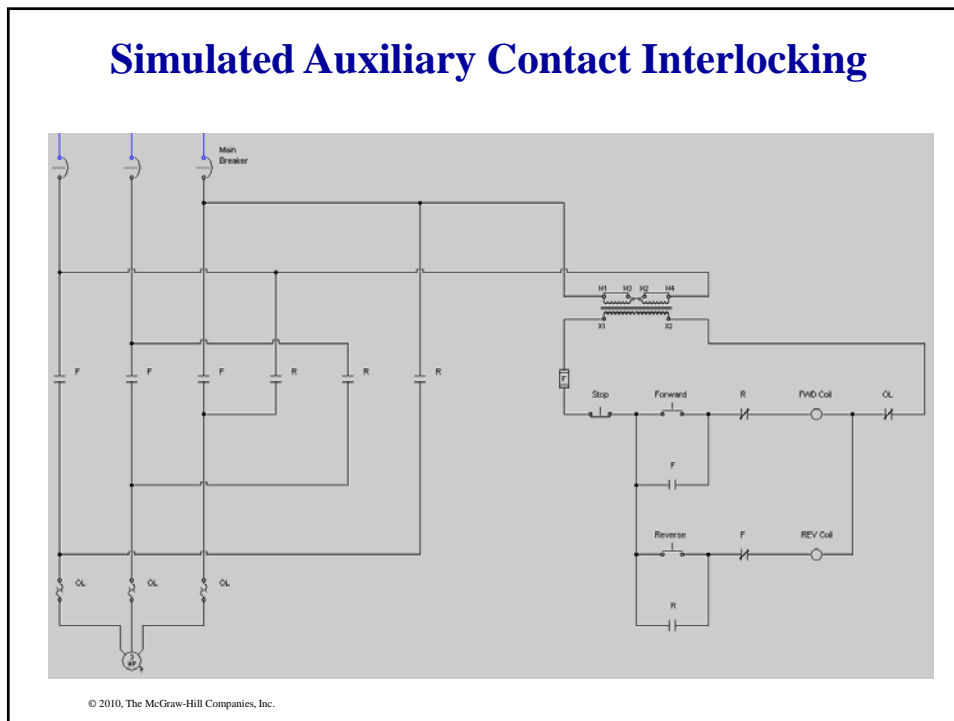


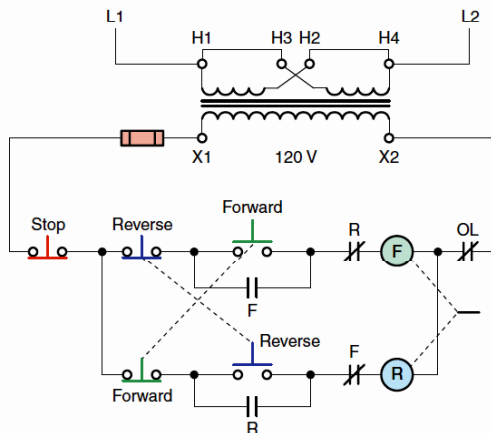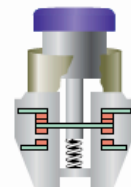Electrical pushbutton interlocking utilizes break-make, normally closed and normally open switch contacts on the forward and reverse buttons.



Interlocking is achieved by connecting the **NC** contact of the **reverse** button in series with the **NO** contact of the **forward** button and vice versa.

© 2010, The McGraw-Hill Companies, Inc.

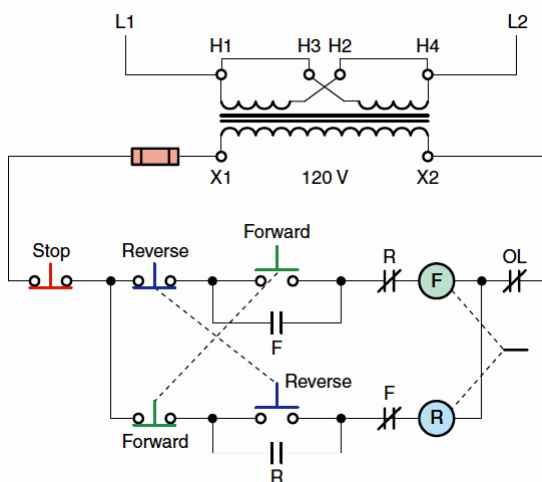

➤ The motor reverses direction immediately without the stop button being pressed.


➤ The NC contact of the reverse button acts like another stop button in the forward circuit.

➤ The NO contact on the reverse button is used as the start button for the reverse circuit.

➤ When the reverse button is pressed, its NC contact opens the circuit to the forward coil and at the same time its NC contact completes the circuit to the reverse coil.


© 2010, The McGraw-Hill Companies, Inc.

Simulated Pushbutton Interlocking

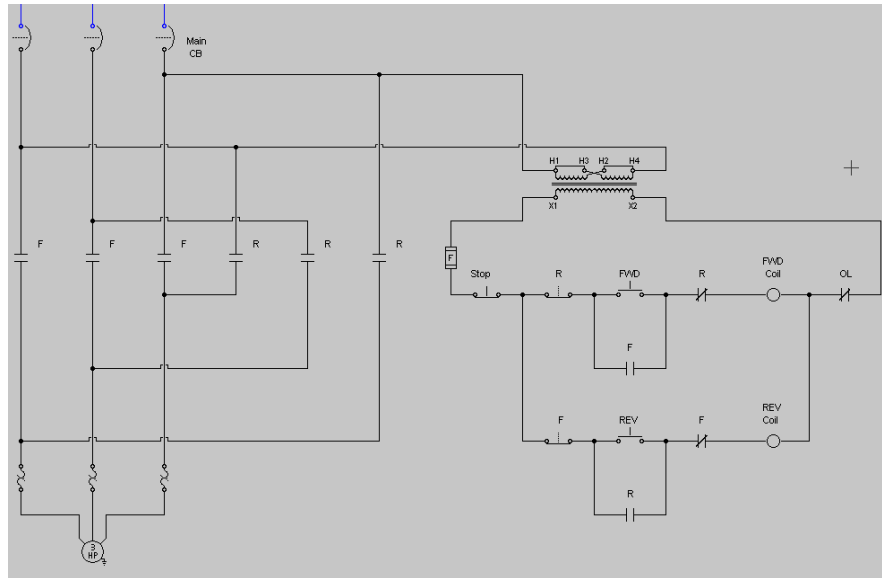

© 2010, The McGraw-Hill Companies, Inc.

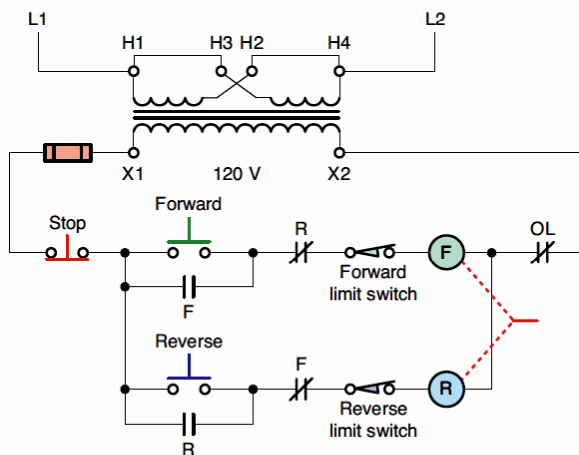
Limit switches can be incorporated into a reversing starter circuit to limit travel.



The location of the limit switches allows the direction of travel to be stopped if the motor is driving a device that has limits to its travel.


© 2010, The McGraw-Hill Companies, Inc.

Simulated Travel Limit Switch Operation

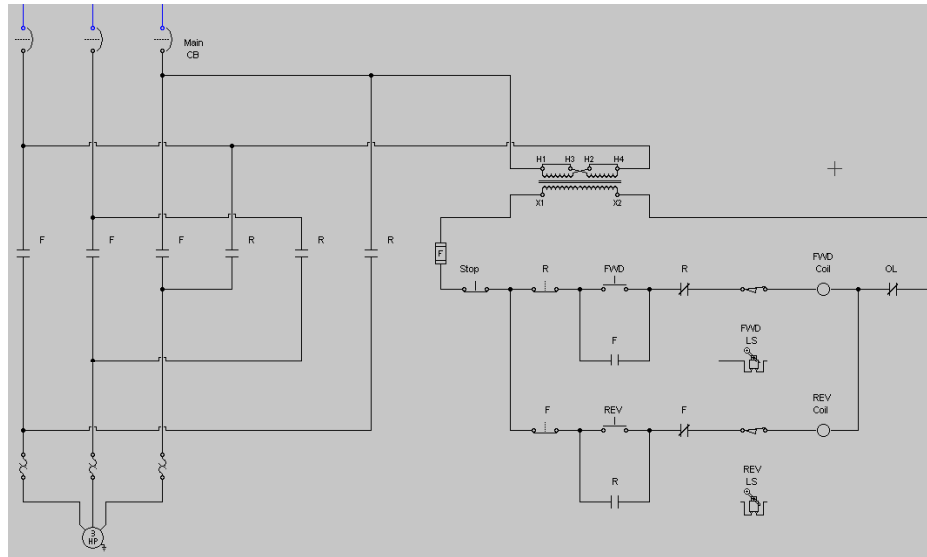

© 2010, The McGraw-Hill Companies, Inc.


Single-Phase Motor Reversing

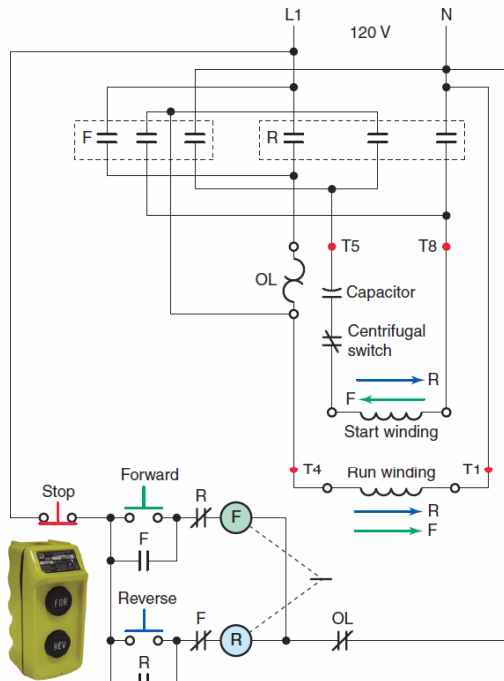


➤ Direction of rotation is changed by interchanging the start winding leads, while those of the run winding remain the same.

➤ The centrifugal switch must be allowed to reclose before any attempt to reverse the direction of rotation

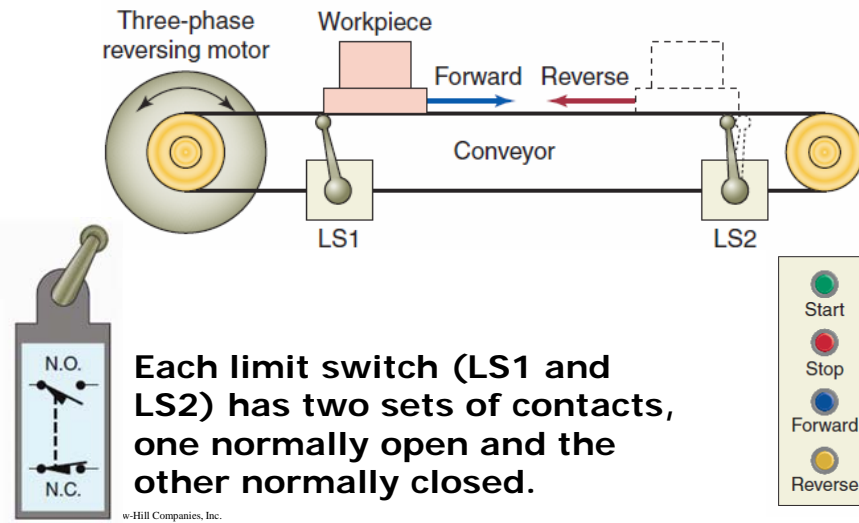Some **reciprocating machine process** use **two limit switches to provide automatic control of the motor.**




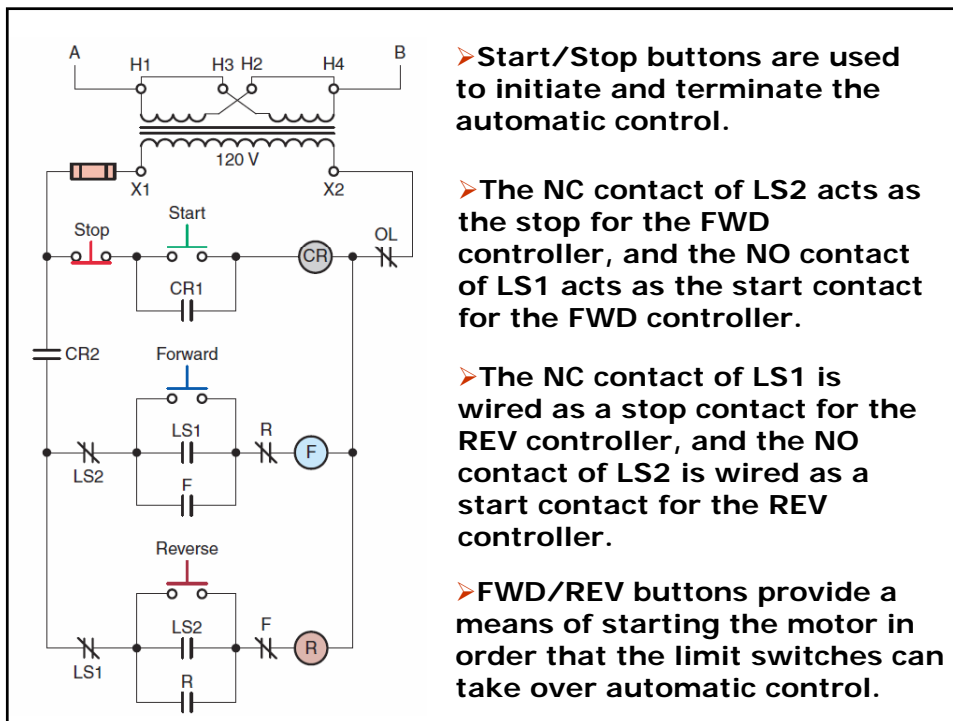Each limit switch (LS1 and LS2) has two sets of contacts, one normally open and the other normally closed.



- Start/Stop buttons are used to initiate and terminate the automatic control.
- The NC contact of LS2 acts as the stop for the FWD controller, and the NO contact of LS1 acts as the start contact for the FWD controller.
- The NC contact of LS1 is wired as a stop contact for the REV controller, and the NO contact of LS2 is wired as a start contact for the REV controller.
- FWD/REV buttons provide a means of starting the motor in order that the limit switches can take over automatic control.


Simulated Reciprocating Machine Process

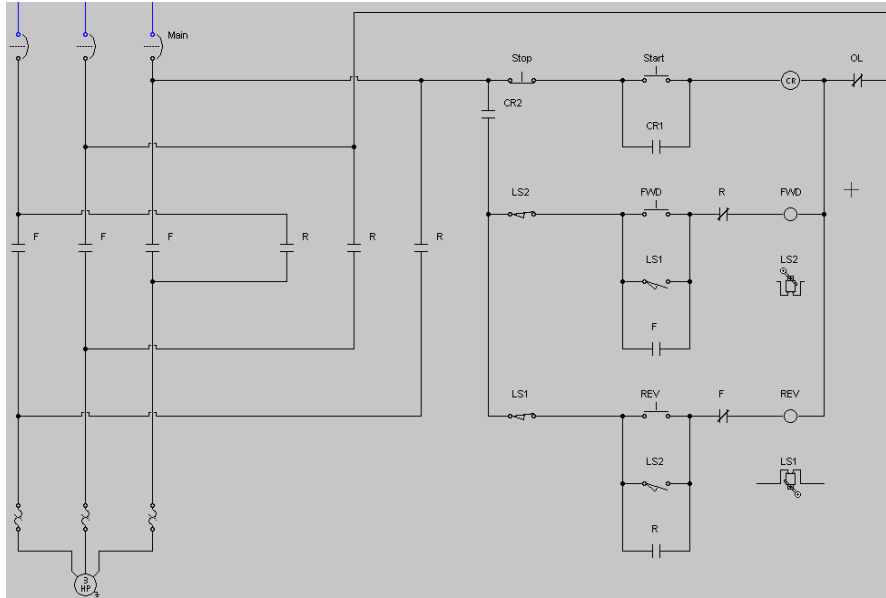

REVERSING OF DC MOTORS

A DC motor is reversed by:

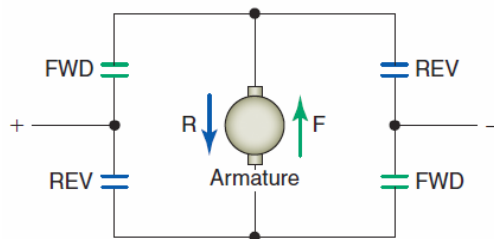
- Reversing the direction of the **armature** current and leaving the field current the same.
- Reversing the direction of the **field** current and leaving the armature current the same.



➤ Most are reversed by switching the direction of current flow through the **armature**.

➤ Since the armature has a much lower inductance than the field **less arcing** occurs at the contacts when reversed in this manner.

© 2010, The McGraw-Hill Companies, Inc.

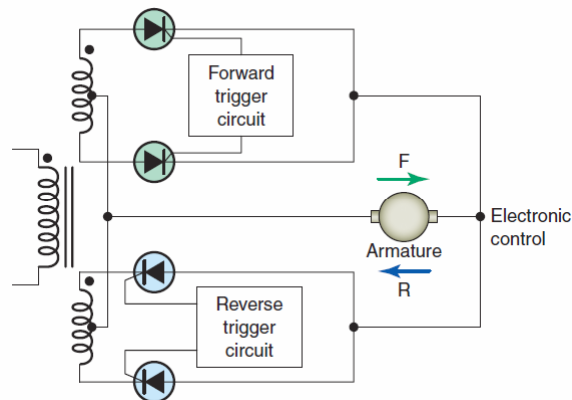

For electronic control, **two sets of SCRs** are provided. One set is used for current flow in one direction through the armature, and the second set is used for current flow in the opposite direction.

© 2010, The McGraw-Hill Companies, Inc.

JOGGING

© 2010, The McGraw-Hill Companies, Inc.

Jogging is the momentary operation of a motor for the purpose of accomplishing small movements of the driven machine.



- Jogging is used for frequent starting and stopping of a motor for short periods of time.
- It involves an operation in which the motor **runs** when the **button is pressed** and will **stop** when the **button is released**.

© 2010, The McGraw-Hill Companies, Inc.

Pushbutton Jog Circuit

➤ With the M coil deenergized and the jog button then pressed, a circuit is completed for the M coil around the M maintaining contact.


- The M main contacts close to start the motor, but the maintaining circuit is incomplete as the NC jog contact is open.
- As a result, starter coil M will not seal in; instead, it can stay energized only as long as the jog button is fully depressed.

© 2010, The McGraw-Hill Companies, Inc.

- On quick release of the jog push button, should its NC contacts reclose before the starter maintaining contact M opens, the motor would continue to run.
- In certain applications this could be hazardous to workers and machinery.

© 2010, The McGraw-Hill Companies, Inc.


Simulated Pushbutton Jog Circuit

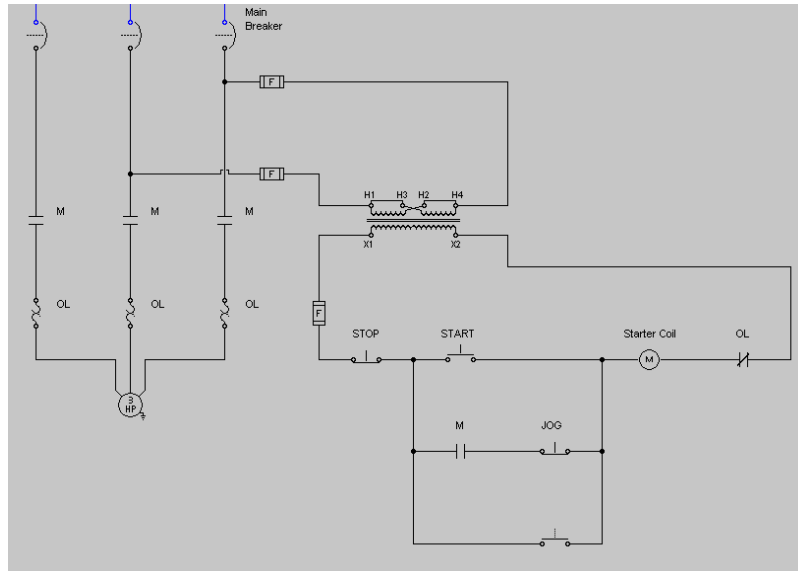

© 2010, The McGraw-Hill Companies, Inc.

A control relay jogging circuit is much safer method of implementing jog control.

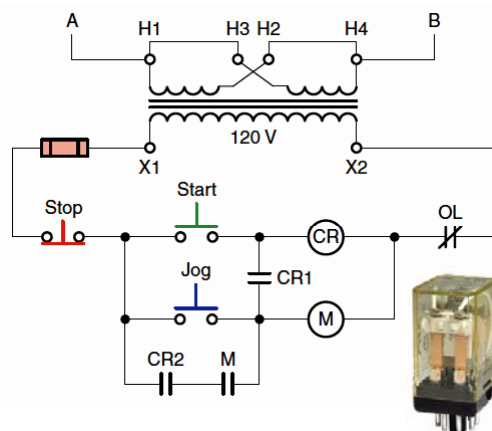
➤ Pressing the **start button** energizes coils CR and M to start and run the motor.



➤ Pressing the **jog button** energizes the M coil only, starting the motor. Both CR contacts remain open, and the CR coil is deenergized. The M coil will not remain energized when the jog push button is released.


© 2010, The McGraw-Hill Companies, Inc.

Simulated Control Relay Jog Circuit

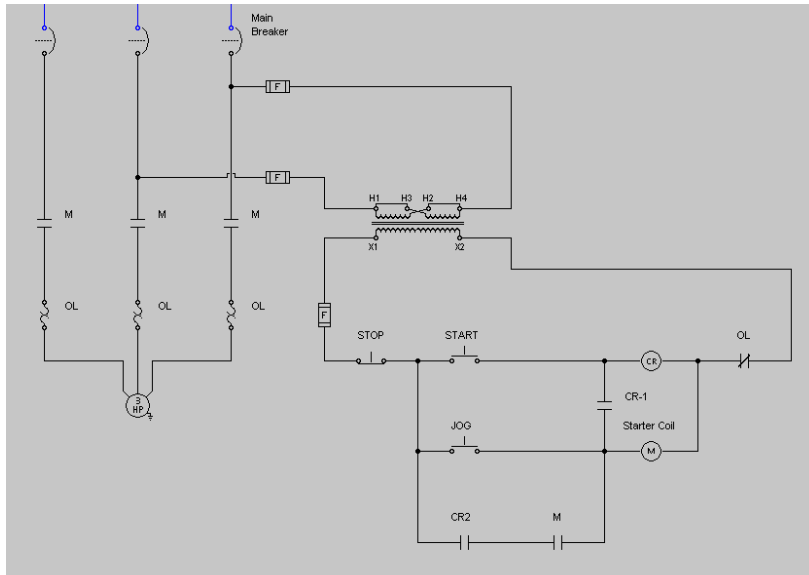

© 2010, The McGraw-Hill Companies, Inc.

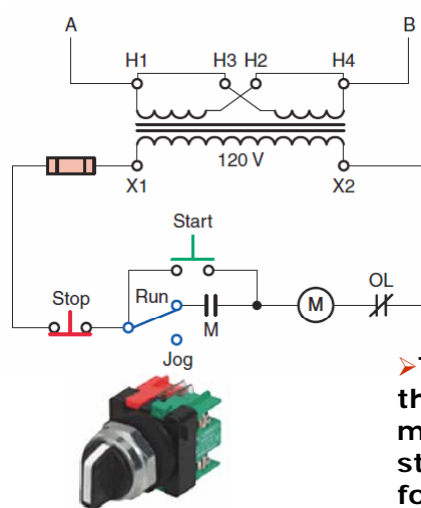A selector switch connected in the control circuit can also be used to implement jogging.




© 2010, The McGraw-Hill Companies, Inc.

➤ The start button doubles as a jog button.

➤ When the selector switch is placed in the run position, the maintaining circuit is not broken. If the start button is pressed, the M coil circuit is completed and maintained.

➤ Turning the selector switch to the jog position opens the maintaining circuit. Pressing the start button completes the circuit for the M coil, but the maintaining circuit is open.

Simulated Selector Switch Jog Circuit

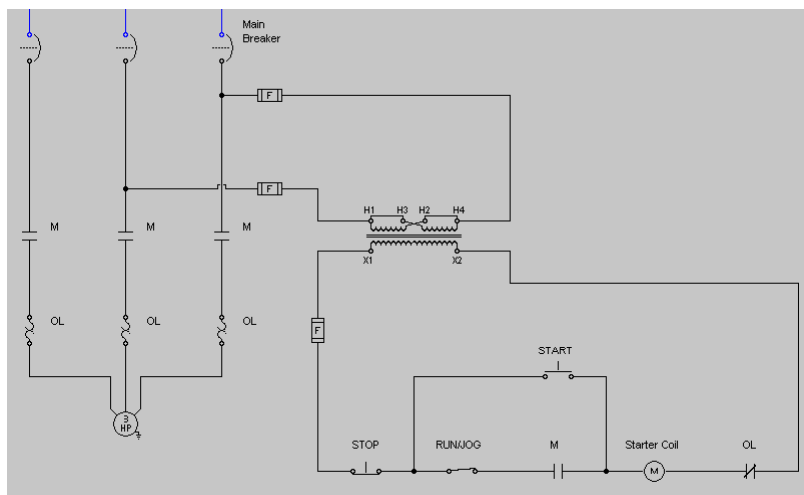

© 2010, The McGraw-Hill Companies, Inc.

The most common method of stopping a motor is to **remove the supply voltage** and allow the motor and load to **coast to a stop**.



In some applications, however, the motor must be stopped more **quickly or held** in position by some sort of braking device.

© 2010, The McGraw-Hill Companies, Inc.

PLUGGING AND ANTI-PLUGGING

© 2010, The McGraw-Hill Companies, Inc.

Plugging stops a polyphase motor quickly, by momentarily connecting the motor for **reverse rotation** while the motor is still running in the forward direction.



Plugging acts as a retarding force for rapid stop and quick reversal of motor rotation.

© 2010, The McGraw-Hill Companies, Inc.

Plugging produces more heat than most normal-duty applications.

NEMA specifications call for reversing starters used for such applications to be **derated**.



The next **size larger** reversing starter must be selected when it is used for plugging to stop or reverse at a rate of more than **five times per minute**.

© 2010, The McGraw-Hill Companies, Inc.

A zero-speed or plugging switch wired into the control circuit of a standard reversing starter can be used for automatic plugging of a motor.





➤ The zero-speed switch is coupled to a moving shaft on the machinery whose motor is to be plugged.

➤ The switch prevents the motor from reversing after it has come to a stop.

➤ As the zero-speed switch rotates, centrifugal force or a magnetic clutch causes its contacts to open or close.


© 2010, The McGraw-Hill Companies, Inc.

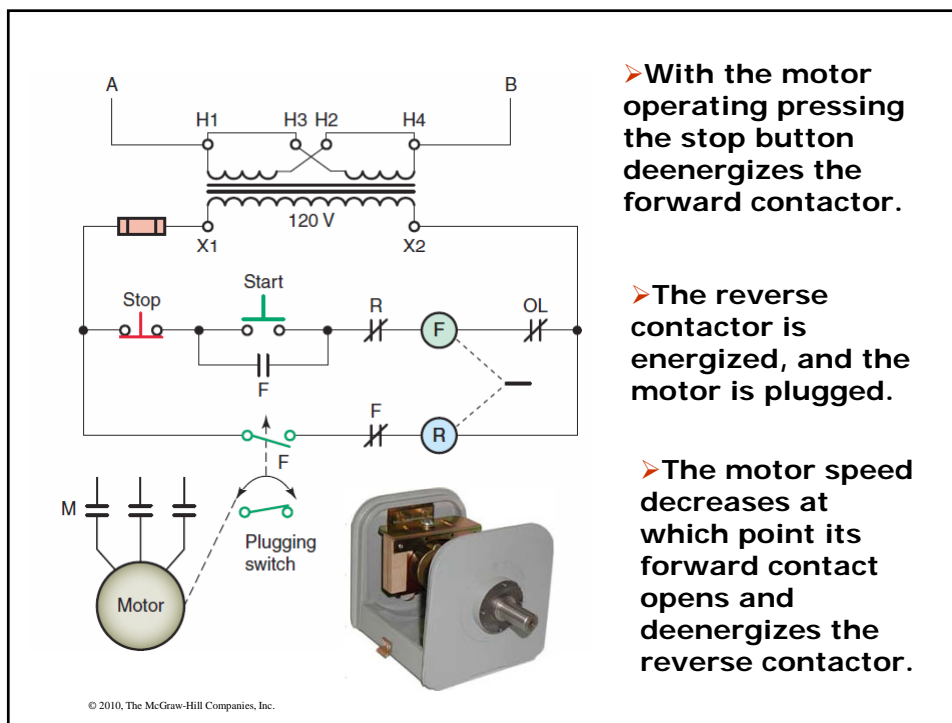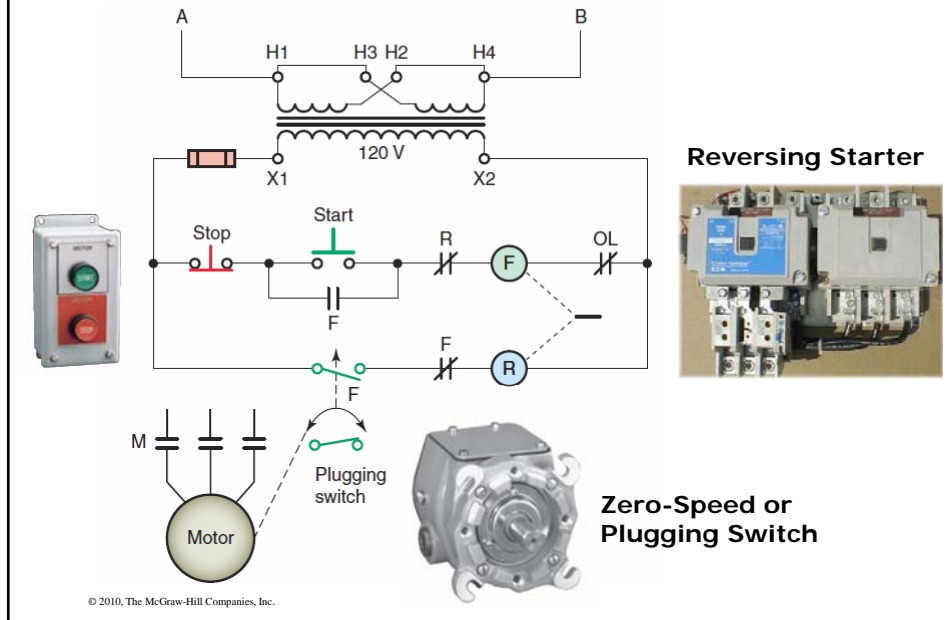Forward direction plugging control circuit.




The sudden reversing torque applied when a **large motor** is reversed (**without slowing the motor speed**) could damage the driven machinery, and the extremely high current could affect the distribution system.

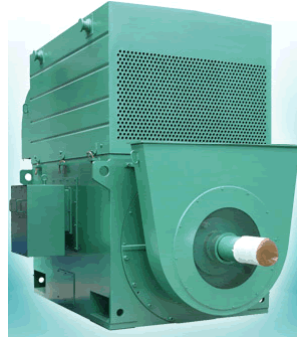Antiplugging protection is obtained when a device prevents the application of a counter torque until the motor speed is reduced to an acceptable value.



© 2010, The McGraw-Hill Companies, Inc.

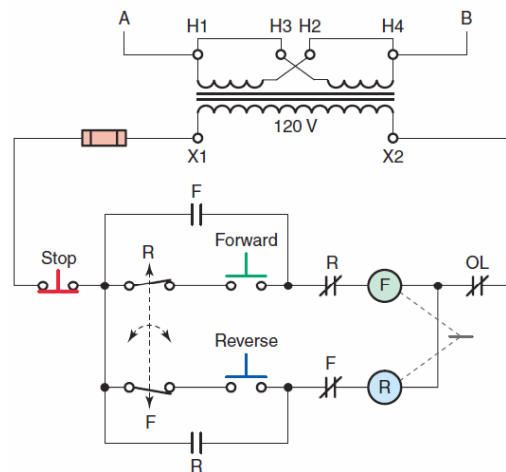Antiplugging circuit used to **prevent reversing** the motor before the motor has slowed to near zero speed.



© 2010, The McGraw-Hill Companies, Inc.

➤ Pressing the forward button completes the circuit for the F coil, closing the F power contacts and causing the motor to run in the forward rotation.

➤ The F zero-speed switch contact opens because of the forward rotation of the motor.

The diagram shows a motor control circuit. A Stop button is connected to the main power line. Two buttons, Forward (F) and Reverse (R), are connected to the Forward (F) and Reverse (R) coils respectively. The Forward coil is protected by a zero-speed switch (ZS) that is normally closed when the motor is running and opens when it reaches zero speed. The Reverse coil is protected by a similar zero-speed switch that is normally open when the motor is running and closes when it reaches zero speed. The Forward and Reverse coils are connected to the motor through power contacts (F and R) and an overload relay (OL). A photograph of a motor control panel and a motor are included for context.

- Pressing the stop button deenergizes the F coil, which opens the F power contacts, causing the motor to slow down.
- Pressing the reverse button will not complete a circuit for the R coil until the F zero-speed switch contact recloses.
- As a result, when the rotating equipment reaches near zero speed, the reverse circuit may be energized, and the motor will run in the reverse rotation.

© 2010, The McGraw-Hill Companies, Inc.

Simulated Anti-Plugging Protection Circuit

This schematic diagram illustrates a simulated anti-plugging protection circuit. It features a main circuit breaker (Main CB) at the top. The main power is distributed to a 3 HP motor and a transformer with primary windings H1, H2, H3, H4 and secondary windings X1, X2. The motor is controlled by Forward (F) and Reverse (R) coils. The Forward coil is energized by a Stop button, a Speed SW - R button, and a FWD button, and is protected by a normally closed contact labeled 'F'. The Reverse coil is energized by a Stop button, a Speed SW - F button, and a REV button, and is protected by a normally open contact labeled 'F'. The circuit also includes a normally open contact labeled 'R' and a normally closed contact labeled 'R'.


© 2010, The McGraw-Hill Companies, Inc.

DYNAMIC BRAKING

© 2010, The McGraw-Hill Companies, Inc.

Dynamic braking is achieved by reconnecting a running motor to act as a generator immediately after it is turned off, rapidly stopping the motor.

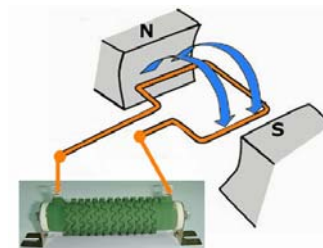The generator action converts the mechanical energy of rotation to electrical energy that can be dissipated as **heat** in a resistor.





Dynamic Braking Resistor

The **smaller** the **ohmic value** of the braking resistor, the greater the rate at which energy is dissipated and the **faster** the motor comes to rest.

© 2010, The McGraw-Hill Companies, Inc.

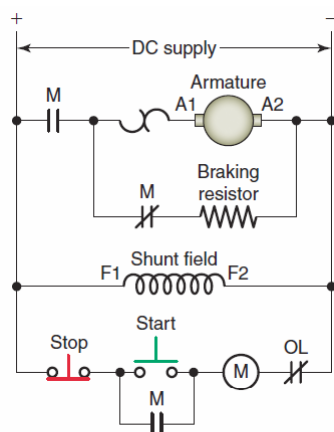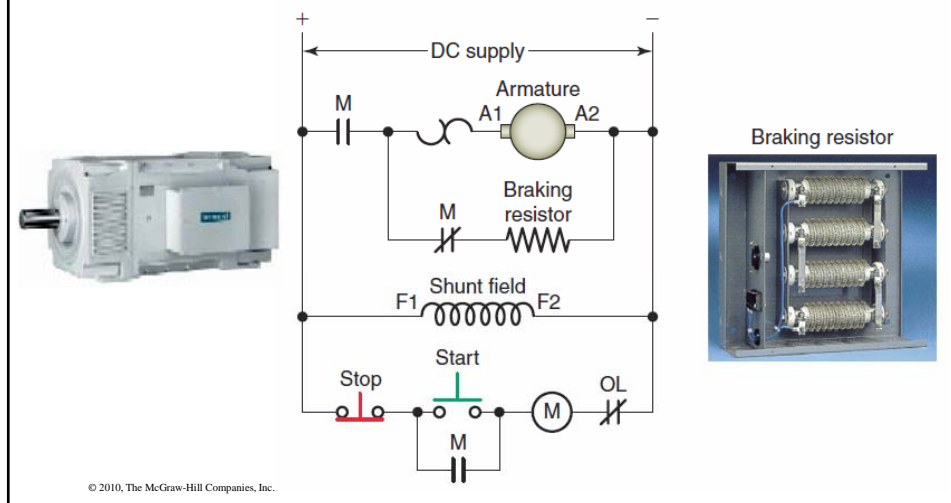Dynamic braking of a DC motor may be needed because DC motors are often used for lifting and moving heavy loads that may be difficult to stop.




- Assume the motor is operating and the stop button is pressed.
- Starter coil M deenergizes to open the normally open M power contact to the motor armature.
- At the same time, the normally closed M power contact closes to complete a braking circuit around the armature through the braking resistor, which acts like a load.
- The shunt field winding of the DC motor remains connected to the power supply.

➤ The armature generates a counter emf voltage. This counter emf causes current to flow through the resistor and armature.

© 2010, The McGraw-Hill Companies, Inc.

Simulated Dynamic Braking Circuit

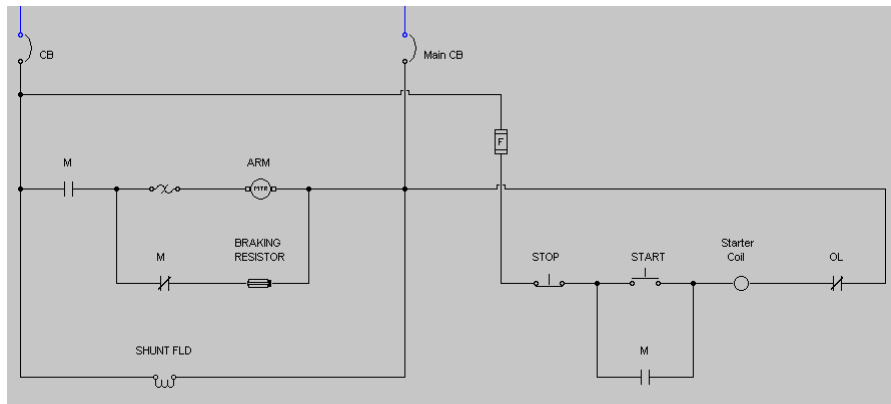


© 2010, The McGraw-Hill Companies, Inc.

DC INJECTION BRAKING

© 2010, The McGraw-Hill Companies, Inc.

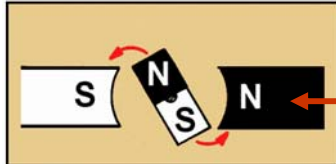DC injection braking is a method of braking in which direct current is applied to the stationary windings of an AC motor after the applied AC voltage is removed.




➤ The injected DC voltage creates a magnetic field in the motor stator winding that does not change in polarity.

➤ In turn, this constant magnetic field in the stator creates a magnetic field in the rotor.



➤ Because the magnetic field of the stator is not changing in polarity, it will attempt to stop the rotor when the magnetic fields are aligned (N to S and S to N).

© 2010, The McGraw-Hill Companies, Inc.

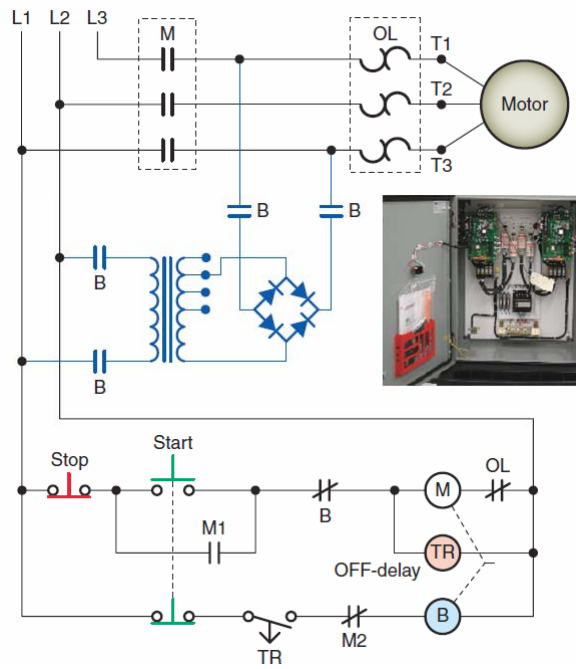
DC injection braking applied to a three-phase AC induction motor.



© 2010, The McGraw-Hill Companies, Inc.

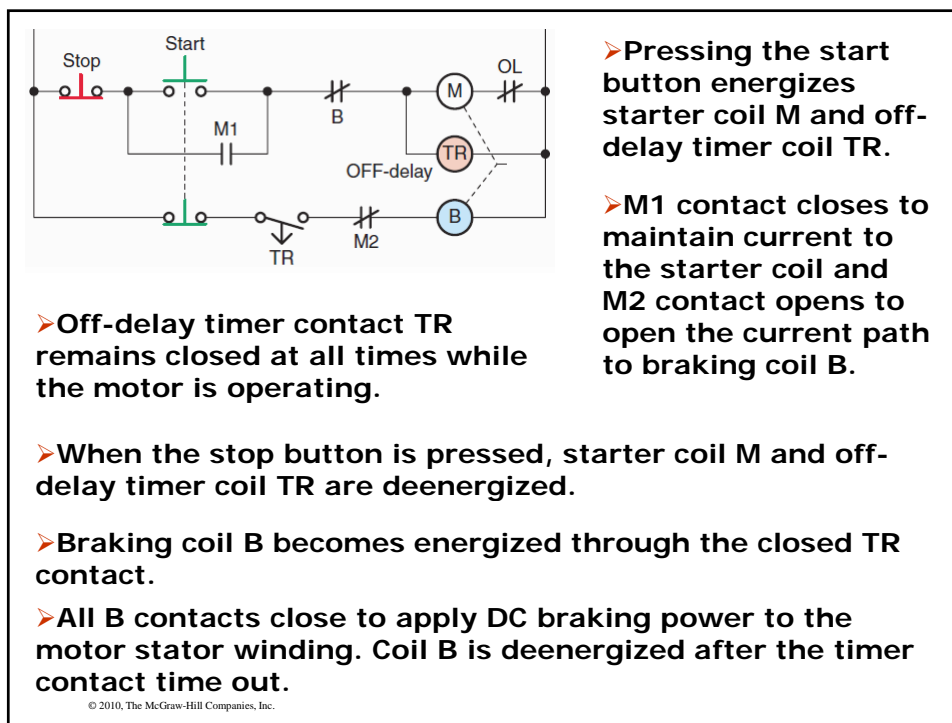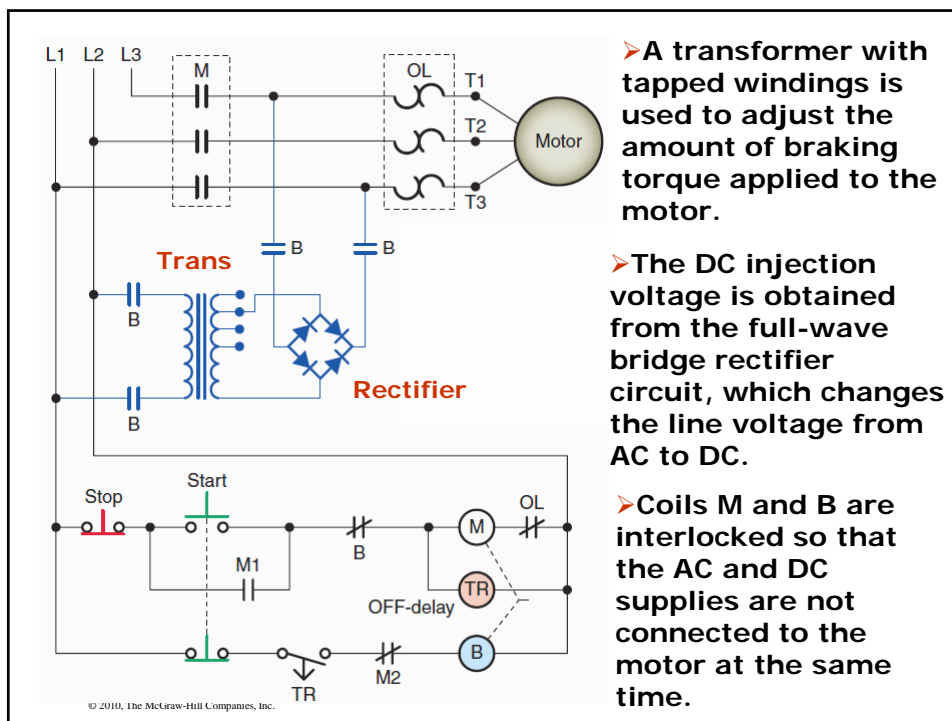

Simulated DC Injection Braking Circuit

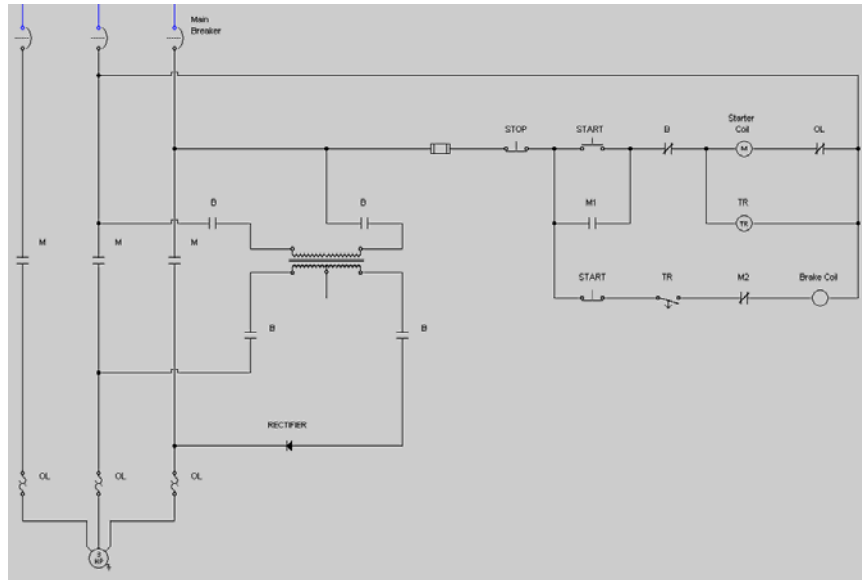


© 2010, The McGraw-Hill Companies, Inc.

ELECTROMECHANICAL FRICTION BRAKES

© 2010, The McGraw-Hill Companies, Inc.

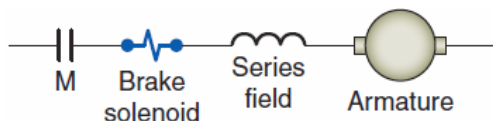
Electromechanical friction brakes can hold the motor shaft stationary after the motor has stopped.



➤ Drum and shoe-type friction brake used on DC series motor drives.

- The brake drum is attached to the motor shaft and the brake shoes are used to hold the drum in place.
- The brake is set with a spring and released by a solenoid.
- When the motor is running, the solenoid is energized to overcome the tension of the spring, thus keeping the brake shoes clear of the drum.



© 2010, The McGraw-Hill Companies, Inc.

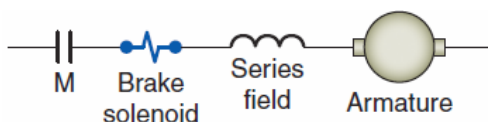

- When the motor is turned off, the solenoid is deenergized and the brake shoes are applied to the drum through the spring tension.
- The brake operating coil is connected in series with the motor armature and release and sets in response to motor current.
- This type of braking is **fail-safe** in that the brake is applied in case of an electrical failure.

© 2010, The McGraw-Hill Companies, Inc.

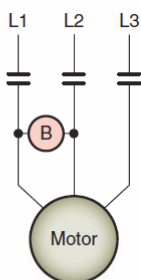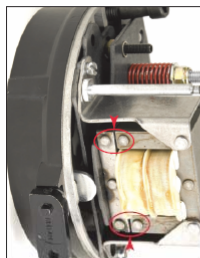AC motor electromagnetic brakes are commonly used as parking brakes to hold a load in place or as stopping brakes to decelerate a load.



➤ These motors are directly coupled to an AC electromagnetic brake.

➤ When the power source is turned off, the motor stops instantaneously and holds the load.


➤ Most come equipped with an external manual release device, which allows the driven load to be moved without energizing the motor.

© 2010, The McGraw-Hill Companies, Inc.

MULTISPEED MOTORS

© 2010, The McGraw-Hill Companies, Inc.

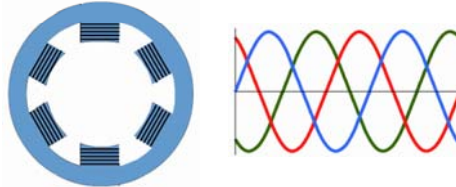The **speed** of an induction motor depends on the number of **poles** built into the motor and the **frequency** of the electrical power supply.





- A single-speed motor has one rated speed at which it runs when supplied with the nameplate voltage and frequency.
- A **multispeed motor** will run at more than one speed, depending on how you connect it to the supply.
- Multispeed motors typically have **two speeds** to choose from, but they may have more.

© 2010, The McGraw-Hill Companies, Inc.

The different speeds of a multispeed motor are selected by connecting the external motor winding stator leads to a multispeed starter.



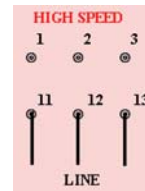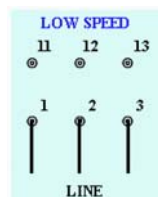
Multispeed magnetic starters automatically reconnect multispeed motor windings for the desired speed in response to a signal received from push button stations or other pilot devices.



© 2010, The McGraw-Hill Companies, Inc.

Multispeed motors are available in two basic versions: consequent pole and separate winding.

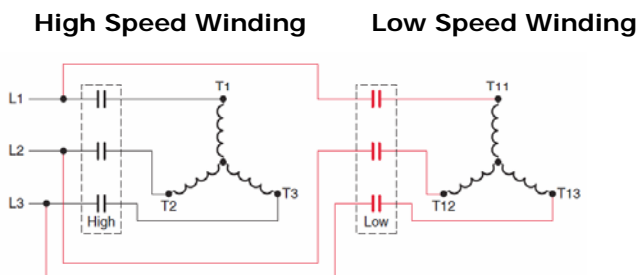
A separate winding motor has a winding for each speed.



- The speed of each winding depends on the number of poles.
- The low-speed winding is wound for more poles than the high-speed winding.
- The motor cost is higher than consequent pole, but the control is simpler.

© 2010, The McGraw-Hill Companies, Inc.

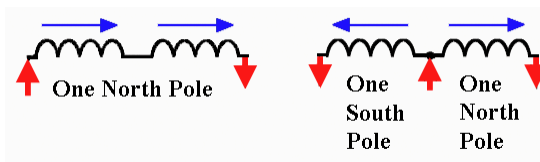
A consequent pole motor has a winding for every two speeds.



- Taps are brought from the winding for reconnection for a different number of poles.
- Two-speed, consequent-pole motors have one reconnectable winding.
- Low speed of a two speed, consequent-pole motor is one half the speed of high speed.
- Three-speed motors have one reconnectable winding and one fixed winding.

© 2010, The McGraw-Hill Companies, Inc.

Two-speed separate winding starter.

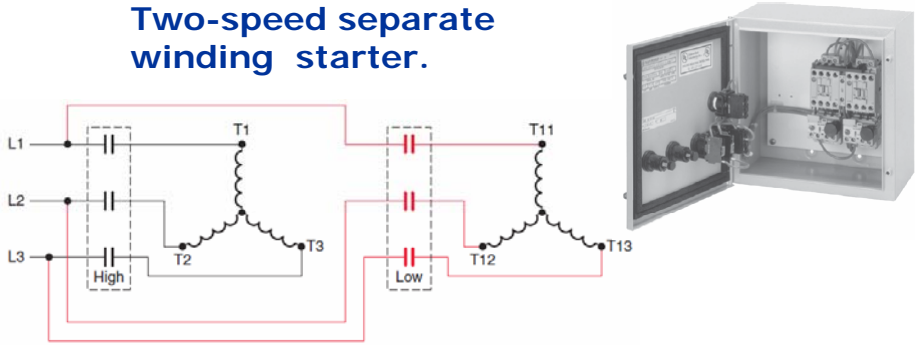


- Contains a high-speed and a low-speed starter, mechanically and electrically interlocked with each other.
- Requires two sets of overload relays, one for the high-speed circuit and one for the low-speed circuit.
- Control panel contains high-speed button, low-speed push , off/high/low selector switch, high-speed OL reset, and low-speed OL reset.

© 2010, The McGraw-Hill Companies, Inc.

WOUND ROTOR MOTORS

© 2010, The McGraw-Hill Companies, Inc.

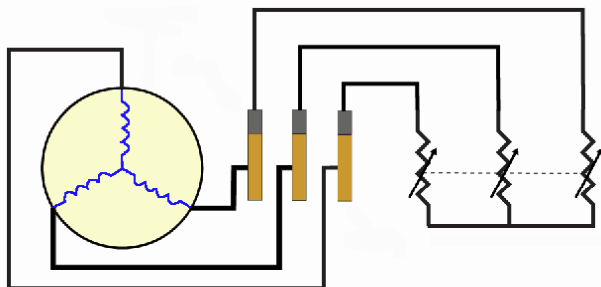A wound rotor motor is constructed with rotor windings that are brought out of the motor through slip rings on the motor shaft.




➤ These windings are connected to a controller, which places variable resistors in series with the windings.

➤ By changing the amount of external resistance connected to the rotor circuit, the motor speed can be varied.

© 2010, The McGraw-Hill Companies, Inc.

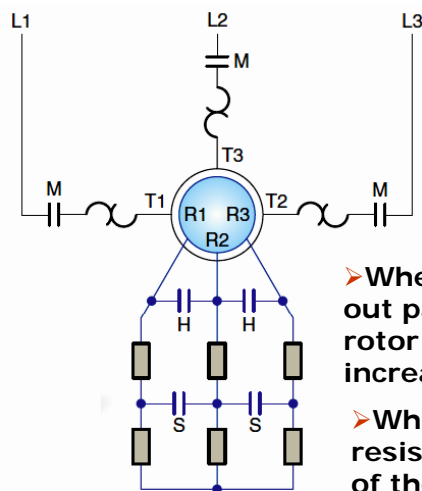Power circuit for a wound-rotor magnetic motor controller.



➤ A magnetic starter (M) connects the primary circuit to the line, and two secondary accelerating contactors (S and H), control the speed.

➤ When operating at low speed, contactors S and H are both open, and full resistance is inserted in the rotor's secondary circuit.

➤ When contactor S closes, it shunts out part of the total resistance in the rotor circuit; as a result, the speed increases.

➤ When contactor H closes, all resistance in the secondary circuit of the motor is bypassed; thus, the motor runs at maximum speed.

© 2010, The McGraw-Hill Companies, Inc.


➤ One disadvantage of using resistance to control the speed of a wound-rotor induction motor is that a lot of heat is dissipated in the resistors; the **efficiency**, therefore, is **low**.

➤ **Speed regulation** is also **poor** when using resistance to control speed; for a given amount of resistance, the speed varies considerably if the mechanical load varies.



➤ Modern wound-rotor controllers use **solid-state devices** to obtain stepless control. These may incorporate thyristors (semiconductors) that serve in the place of magnetic contactors.

© 2010, The McGraw-Hill Companies, Inc.

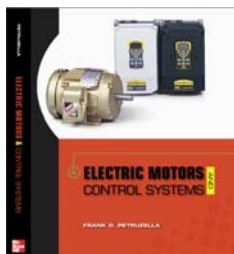

Chapter 8

Motor Control Circuits

© 2010, The McGraw-Hill Companies, Inc.